

- Name :- Kanada Prakhar T.
- Subject :- Digital System Design (3EL42)
- ID No. :- 21EL041
- Division :-04
- Branch :- Electronics Department
- Year :- 2023-24

Assignment 3

1. Clock Divider

Verilog code:

```
module clock_divider(  
    input rst,  
    input  clk,  
  
    output reg div_by_2,div_by_4,div_by_8,div_by_16  
  
    );  
    reg [3:0]count;  
    always @ (posedge clk)  
  
    begin  
        if(rst==0)  
            count=4'b0000;  
  
        else  
  
            count = count + 1;  
  
            div_by_2  = count[0];  
            div_by_4  = count[1];  
            div_by_8  = count[2];  
            div_by_16 = count[3];  
  
    end  
endmodule
```

Testbench:

```

module clock_divider_tb(

);
  reg clk;
  reg rst;
  wire div_by_2,div_by_4,div_by_8,div_by_16;

  clock_divider uut(rst,clk,div_by_2,div_by_4,div_by_8,div_by_16);
  initial      clk = 1'b0;
              always #5 clk = ~clk;

  initial begin : test

      rst = 1'b0;
      #10
      rst = 1'b1;


      #60000
      $finish;

  end


endmodule

```

Simulation:

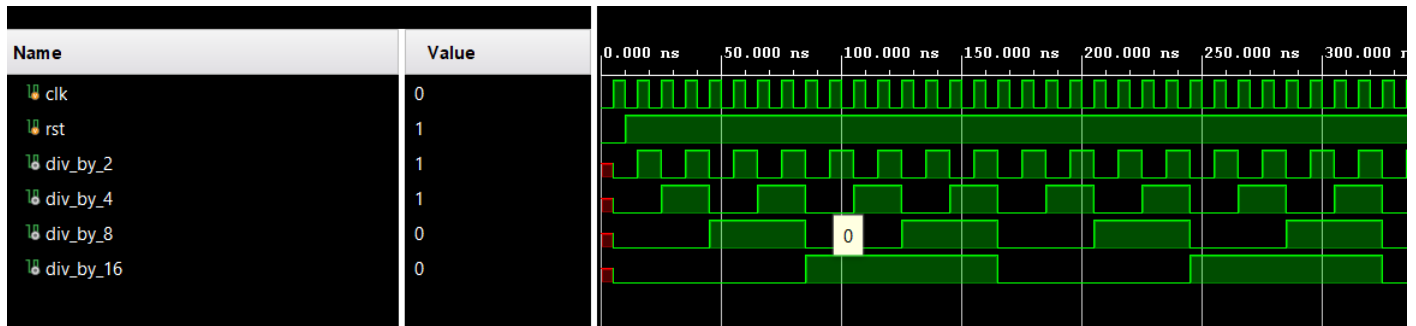

Schematic:

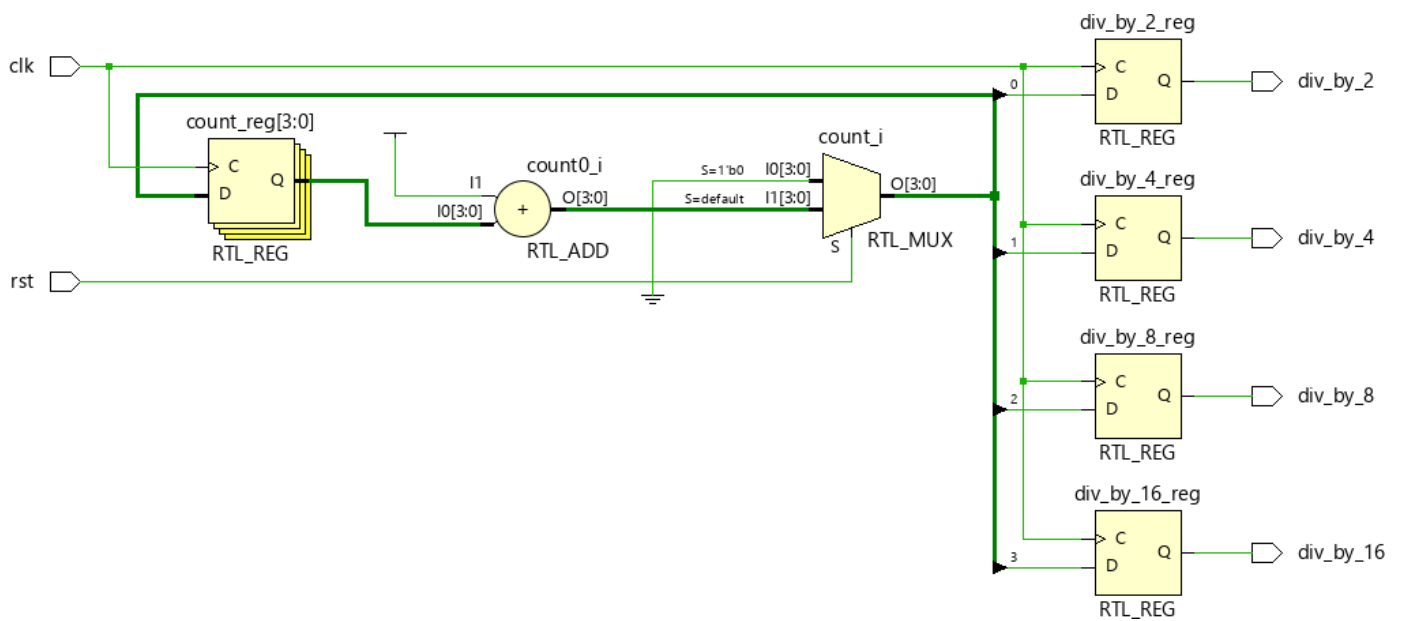

Synthesis report:

Start Writing Synthesis Report

Report BlackBoxes:

```
++-----+
| |BlackBox name |Instances |
++-----+
++-----+
```

Report Cell Usage:

```
++-----+
| |Cell |Count |
++-----+
|1 |BUFG | 1|
|2 |LUT1 | 2|
|3 |LUT2 | 1|
|4 |LUT3 | 1|
|5 |LUT4 | 1|
|6 |FDRE | 4|
|7 |IBUF | 2|
|8 |OBUF | 4|
++-----+
```

Report Instance Areas:

```
++-----+
| |Instance |Module |Cells |
++-----+
|1 |top      |      | 16|
++-----+
```

Finished Writing Synthesis Report : !


Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: **3.777 W**
Design Power Budget: **Not Specified**
Power Budget Margin: **N/A**
Junction Temperature: **32.1°C**
Thermal Margin: 52.9°C (27.9 W)
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: **Low**

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

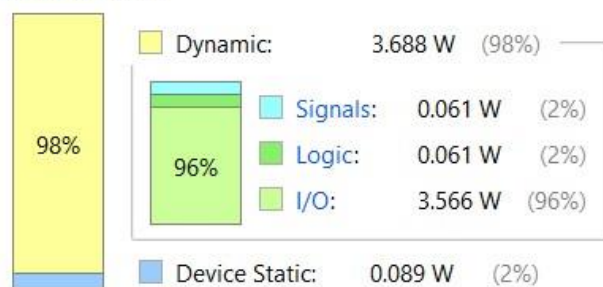

2. Johnson Counter

Verilog code:

```
module johnson_counter( out,reset,clk);
input clk,reset;
output [3:0] out;

reg [3:0] q;

always @(posedge clk)
begin

if(reset)
q=4'd0;
else
begin
q[3]<=q[2];
q[2]<=q[1];
q[1]<=q[0];
q[0]<=(~q[3]);
end
end

assign out=q;
endmodule
```

Testbench:

```
module jc_tb;
reg clk,reset;
wire [3:0] out;

johnson_counter dut (.out(out), .reset(reset), .clk(clk));


always
#5 clk =~clk;

initial begin
reset=1'b1; clk=1'b0;
#20 reset= 1'b0;
end


initial
begin
$monitor( $time, " clk=%b, out= %b, reset=%b", clk,out,reset);
#105 $stop;
end

endmodule
```

Simulation:

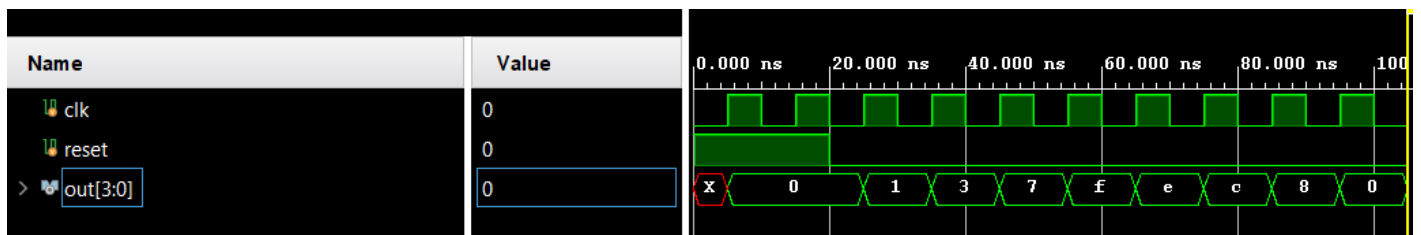

Schematic:

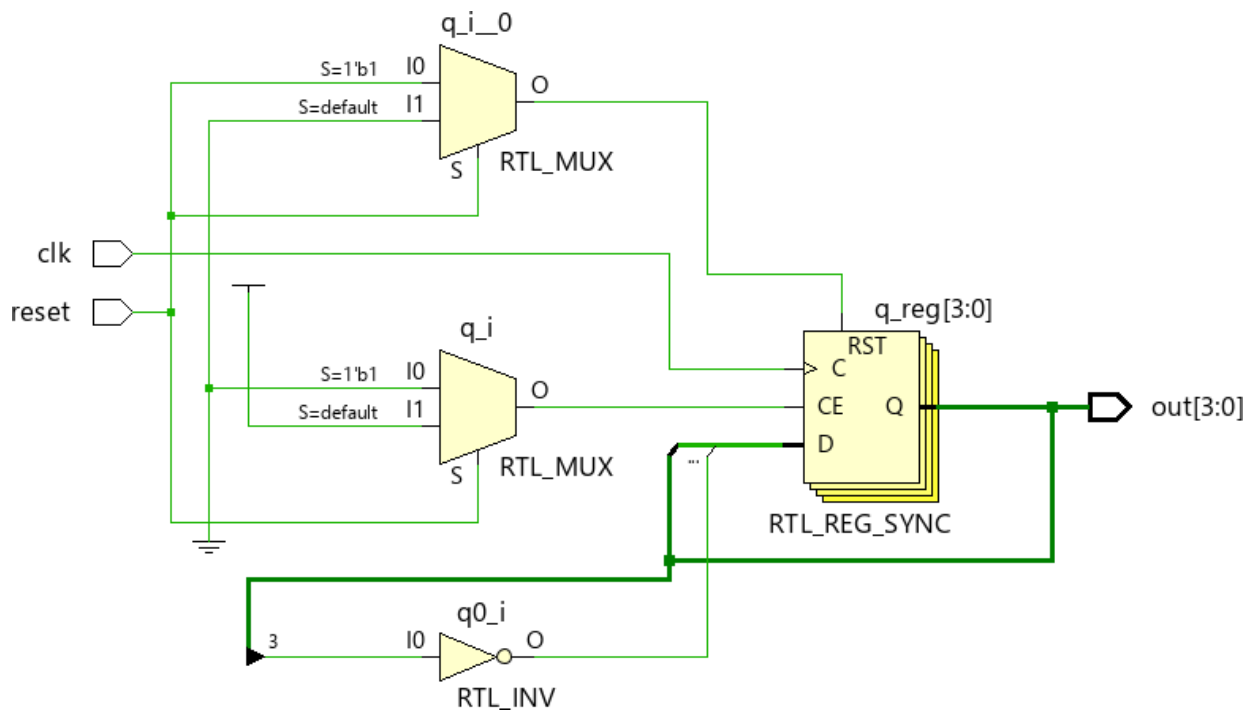

Synthesis report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

	Cell	Count
1	BUFG	1
2	LUT1	1
3	FDRE	4
4	IBUF	2
5	OBUF	4

Report Instance Areas:

Instance	Module	Cells
1	top	12

Finished Writing Synthesis Report :

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:

1.074 W

Design Power Budget:

Not Specified

Power Budget Margin:

N/A

Junction Temperature:

27.0°C

Thermal Margin:

58.0°C (30.6 W)

Effective ΘJA:

1.9°C/W


Power supplied to off-chip devices:

0 W

Confidence level:

Low

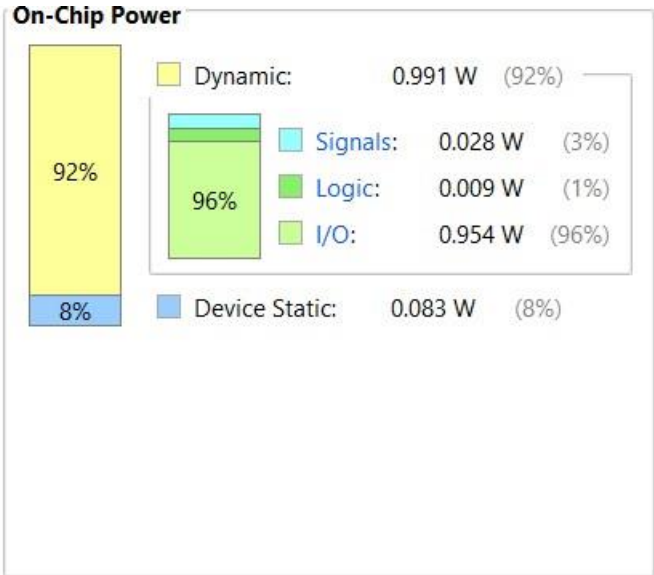[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



3. Ring Counter


Verilog code:

```
module ring_counter(  
    input clk,  
    input rst,  
    output reg [3:0] q  
);  
  
    always @(posedge clk)  
    begin  
        if(rst==1)  
  
            q <= 4'b0001;  
  
        else  
            begin  
                q[0]<=q[3];  
                q[1]<=q[0];  
                q[2]<=q[1];  
                q[3]<=q[2];  
            end  
        end  
    end  
endmodule
```


Testbench:

```
module ring_counter_tb(  
  
);  
  
    reg clk;  
    reg rst;  
    wire [3:0]q;  
  
    ring_counter uut(clk,rst,q);  
  
    initial begin  
        #0 clk=1'b0;  
        #0 rst = 1'b0;  
    end  
  
    always  
    #10 clk = ~clk;  
    initial  
    begin  
        #10 rst =1'b1;  
        #20 rst =1'b0;  
        #500 $finish;  
    end  
  
endmodule
```

Simulation:

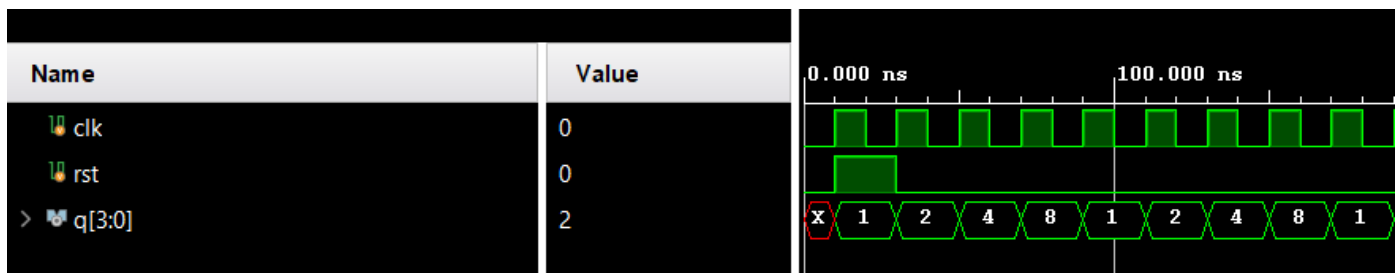

Schematic:

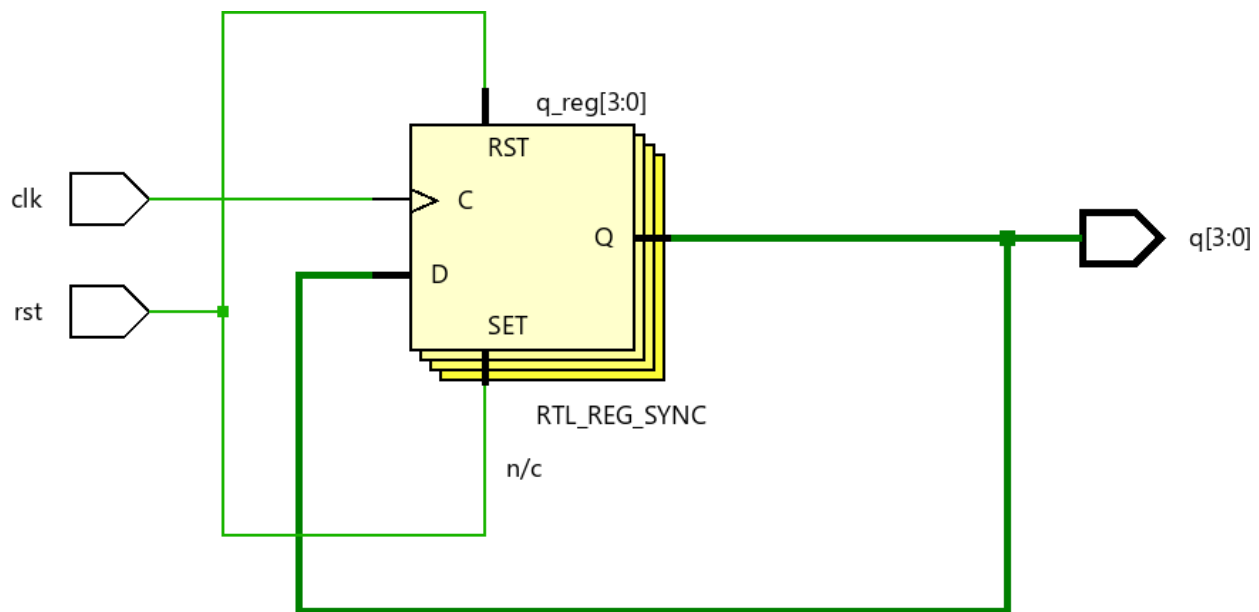

Synthesis report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name Instances		

Report Cell Usage:

Cell Count		
1	BUFG	1
2	FDRE	3
3	FDSE	1
4	IBUF	2
5	OBUF	4

Report Instance Areas:

Instance Module Cells		
1	top	11


Finished Writing Synthesis Report

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	1.069 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	27.0°C
Thermal Margin:	58.0°C (30.6 W)
Effective θJA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

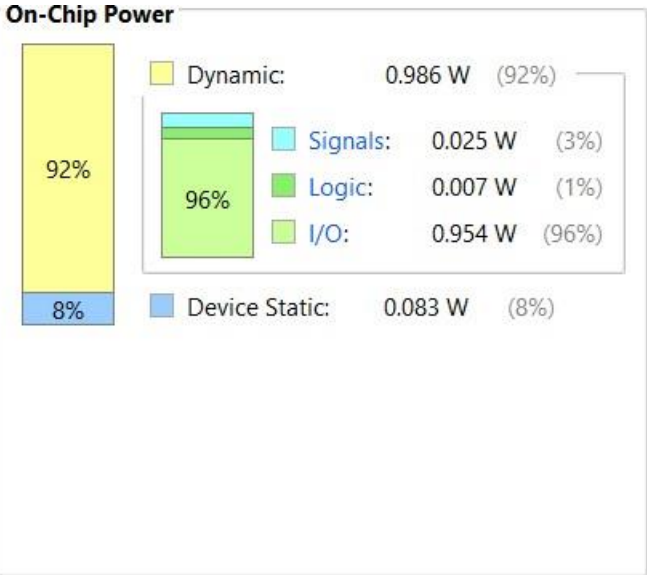[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



4. 5 Input Majority circuit

Verilog code:

```
module majority_of_five(input [4:0] sw, output led);

assign led = (sw[0] & sw[1] & sw[2]) |
             (sw[0] & sw[1] & sw[3]) |
             (sw[0] & sw[1] & sw[4]) |
             (sw[0] & sw[2] & sw[3]) |
             (sw[0] & sw[2] & sw[4]) |
             (sw[0] & sw[3] & sw[4]) |
             (sw[1] & sw[2] & sw[3]) |
             (sw[1] & sw[2] & sw[4]) |
             (sw[1] & sw[3] & sw[4]) |
             (sw[2] & sw[3] & sw[4]);

endmodule
```

Testbench:

```
module majority_of_five_tb;

reg [4:0] sw;
wire led;

majority_of_five cut (.sw(sw),.led(led));


integer k;

initial
begin
    sw = 0;


    for (k=0; k<32; k=k+1)
        #20 sw = k;

    #20 $finish;
end
endmodule
```

Simulation:

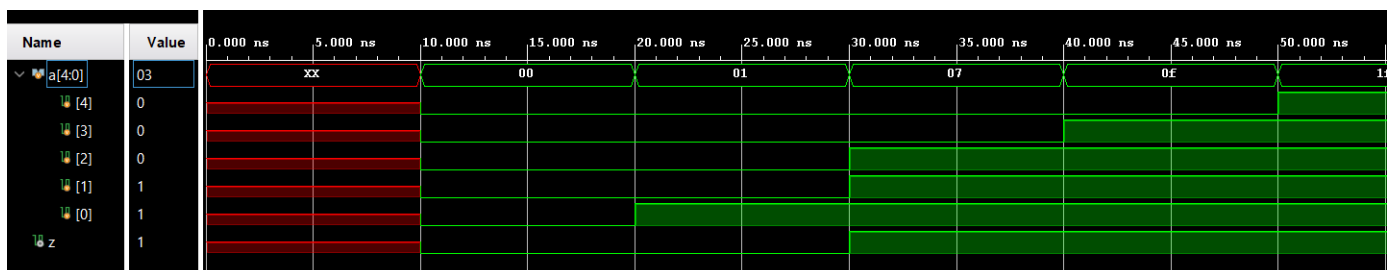

Schematic:

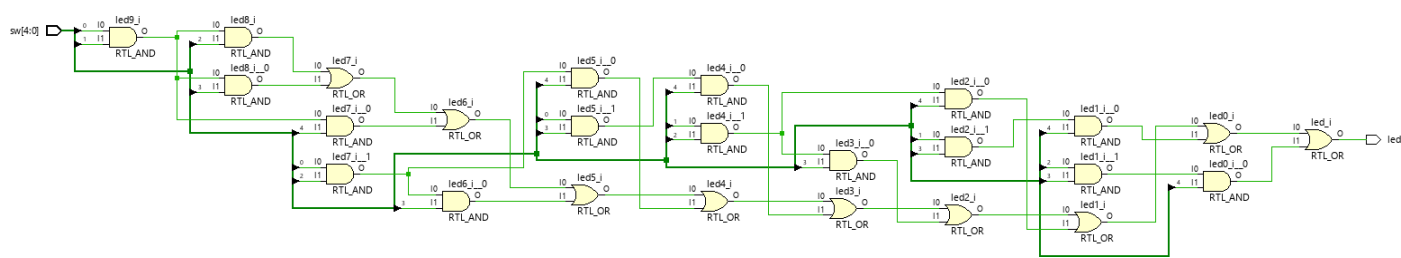

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| |BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| |Cell |Count |
+-----+
|1 |LUT5 | 1|
|2 |IBUF | 5|
|3 |OBUF | 1|
+-----+

Report Instance Areas:
+-----+
| |Instance |Module |Cells |
+-----+
|1 |top      |      | 7|
+-----+

Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.478 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 25.9°C


Thermal Margin: 59.1°C (31.2 W)

Effective θ JA: 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: [Low](#)

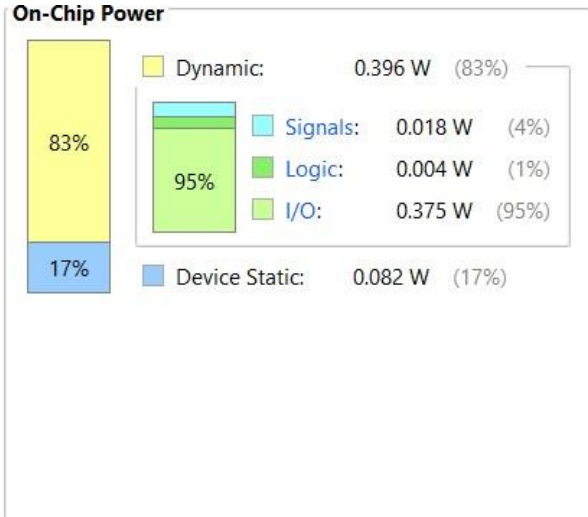[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



5. Parity Generator


Verilog code:

```
module parity_genrator(  
    input x,  
    input y,  
    input z,  
    output out  
);  
  
    xor (out,x,y,z);  
  
endmodule
```


Testbench:

```
module parity_genrator_tb(  
  
);  
    reg x,y,z;  
    wire out;  
  
    parity_genrator uut(x,y,z,out);  
  
    initial  
    begin  
  
        #00  x=0 ; y=0 ; z=0;  
        #100 x=0 ; y=0 ; z=1;  
        #100 x=0 ; y=1 ; z=0;  
        #100 x=0 ; y=1 ; z=1;  
        #100 x=1 ; y=0 ; z=0;  
        #100 x=1 ; y=0 ; z=1;  
        #100 x=1 ; y=1 ; z=0;  
        #100 x=1 ; y=1 ; z=1;  
        #100 x=0 ; y=0 ; z=0;  
    end  
  
    initial begin  
  
        $dumpfile("dump.vcd");  
        $dumpvars(0);  
  
    end  
endmodule
```

Simulation:

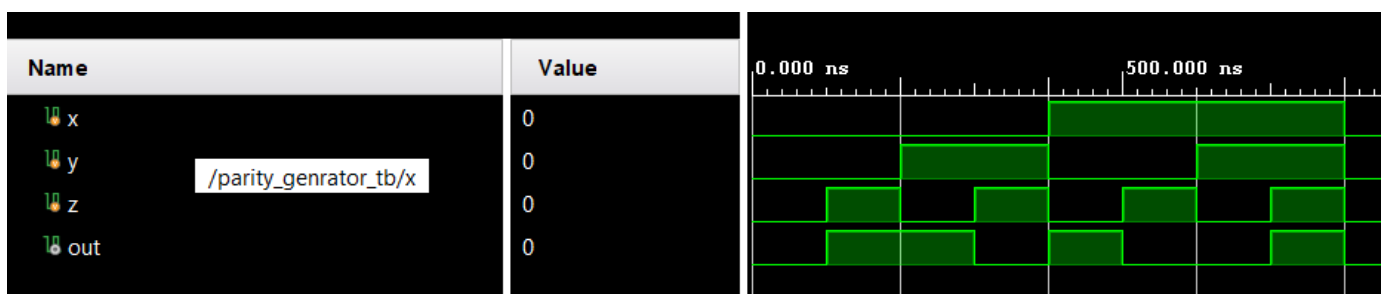

Schematic:

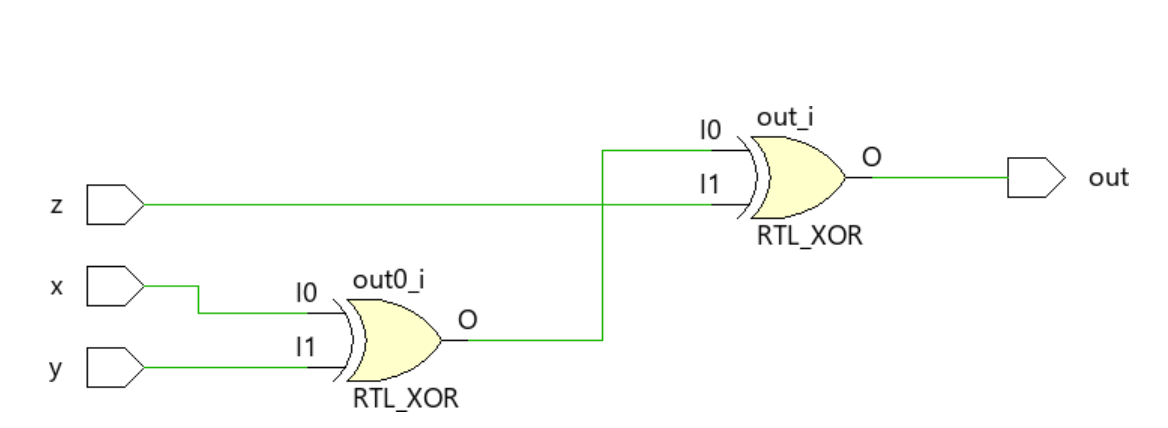

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
| 1    |LUT3  | 1    |
| 2    |IBUF  | 3    |
| 3    |OBUF  | 1    |
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
| 1        |top    |      | 5    |
+-----+

Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.661 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 26.2°C


Thermal Margin: 58.8°C (31.0 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

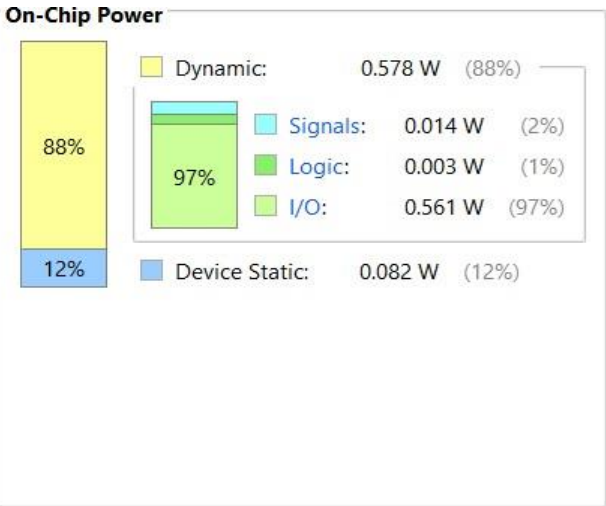[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



6. Binary to one hot encoder

Verilog code:

```
`timescale 1ns / 1ps

module binary_to_one_hot_encoder(
    input [3:0] a,
    output [15:0] b
);

    assign b = 1'b1 <<a;

endmodule
```

Testbench:

```
`timescale 1ns / 1ps

module binary_to_one_hot_encoder_tb;
    reg [3:0] a;
    wire [15:0] b;

    binary_to_one_hot_encoder uut(a,b);

    initial begin

        #10 a=4'b0000;
        #10 a=4'b0001;
        #10 a=4'b0010;
        #10 a=4'b0011;
        #10 a=4'b0100;
        #10 a=4'b0101;
        #10 a=4'b0110;
        #10 a=4'b0111;
        #10 a=4'b1000;
        #10 a=4'b1001;
        #10 a=4'b1010;
        #10 a=4'b1011;
        #10 a=4'b1100;
        #10 a=4'b1101;
        #10 a=4'b1110;
        #10 a=4'b1111;

    end

    initial begin

        $dumpfile("dump.vcd");
        $dumpvars(0);


    end

endmodule
```


Simulation:

Name	Value	0.000 ns		20.000 ns		40.000 ns		60.000 ns		80.000 ns		100.000 ns		120.000 ns		140.000 ns		160.000 ns		180.000 ns	
> a[3:0]	f	x	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e			f	
> b[15:0]	8000	xxxx	0001	0002	0004	0008	0010	0020	0040	0080	0100	0200	0400	0800	1000	2000	4000			8000	

Schematic:

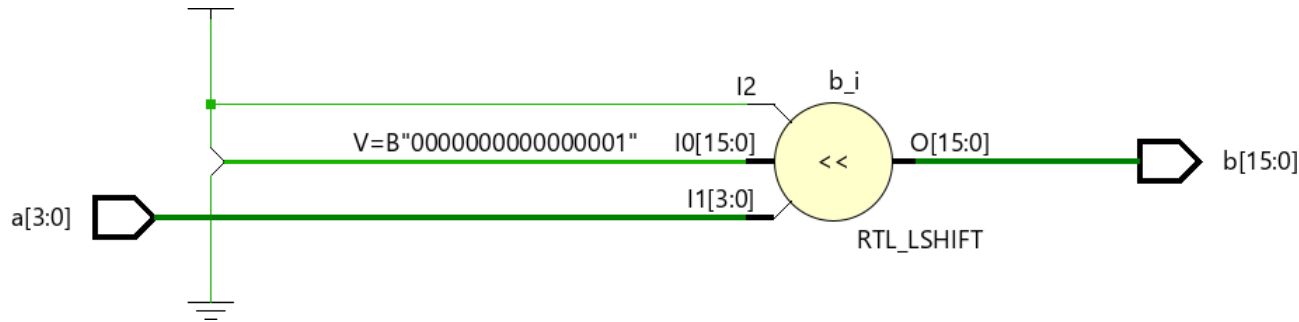

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |LUT4 |    16|
|2      |IBUF |     4|
|3      |OBUF |    16|
+-----+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
|1      |top      |      |    36|
+-----+-----+-----+-----+
-----


Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	1.765 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	28.3°C
Thermal Margin:	56.7°C (29.9 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

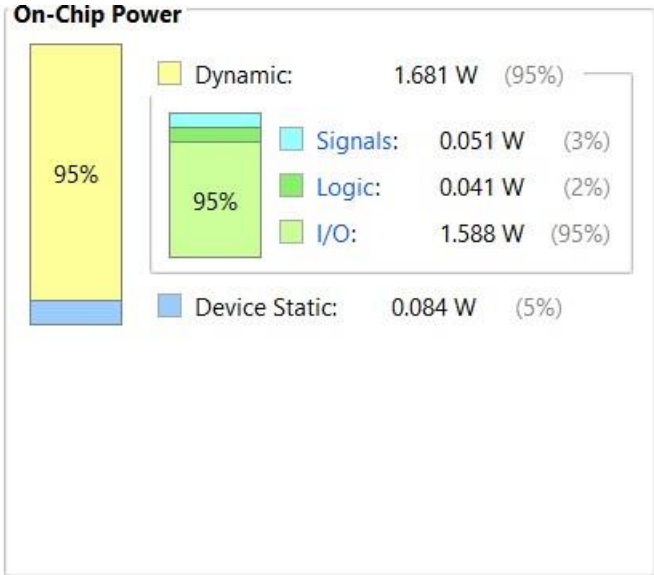[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



7. 4-Bit BCD Synchronous Counter

Verilog code:

```
`timescale 1ns / 1ps

module bcd_4_bit_synchronous_counter(
    input clk,
    input rst,
    output reg [3:0] count
);
    reg [3:0] t;
    always @ (posedge clk)
    begin
        if (rst)
        begin
            t <= 4'b0000;
            count <= 4'b0000;
        end
        else
        begin
            t <= t + 1;
            if (t == 4'b1001)
            begin
                t <= 4'b0000;
            end
            count <= t;
        end
    end
endmodule
```

Testbench:

```
`timescale 1ns / 1ps


module bcd_4_bit_synchronous_counter_tb(
);
    reg clk;
    reg rst;
    wire [3:0] count;

    bcd_4_bit_synchronous_counter uut(clk,rst,count);


    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    initial begin
        rst = 1;
        #10 rst = 0;
        $monitor ("T=%0t out=%b", $time, count);
        #150 rst = 1;
        #10 rst = 0;
        #200
        $finish;
    end
endmodule
```

Simulation:

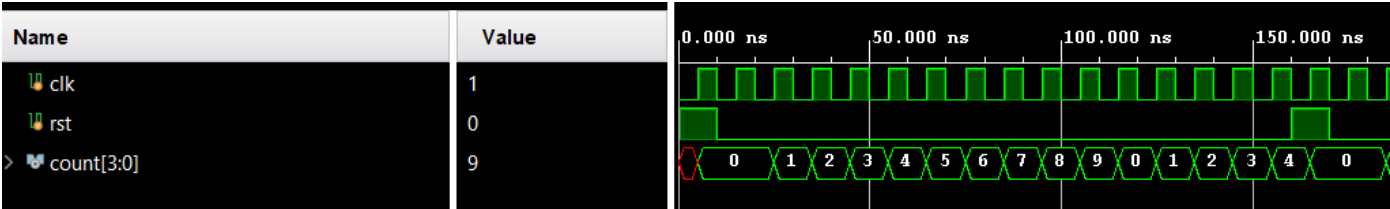

Schematic:

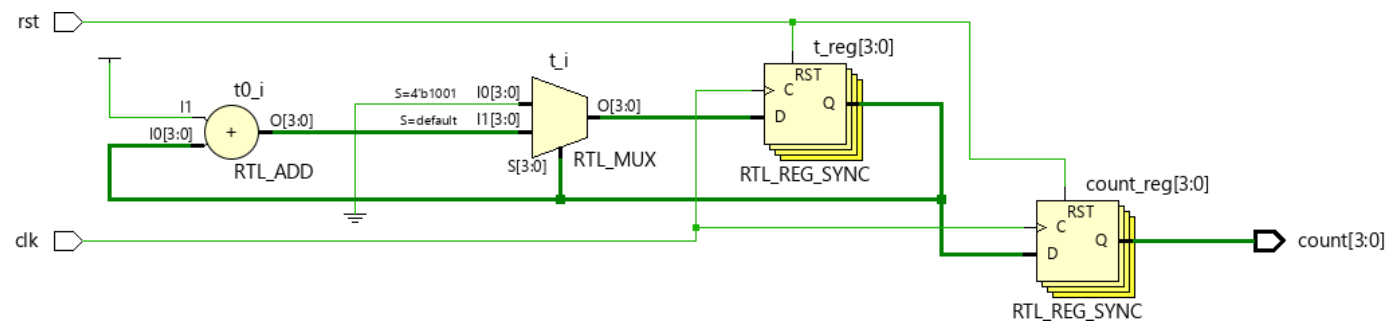

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
| 1     |BUFG |    1|
| 2     |LUT1 |    1|
| 3     |LUT3 |    1|
| 4     |LUT4 |    2|
| 5     |FDRE |    8|
| 6     |IBUF |    2|
| 7     |OBUF |    4|
+-----+-----+-----+


Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
| 1     |top      |      |    19|
+-----+-----+-----+-----+
-----
Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	3.609 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	31.8°C
Thermal Margin:	53.2°C (28.1 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

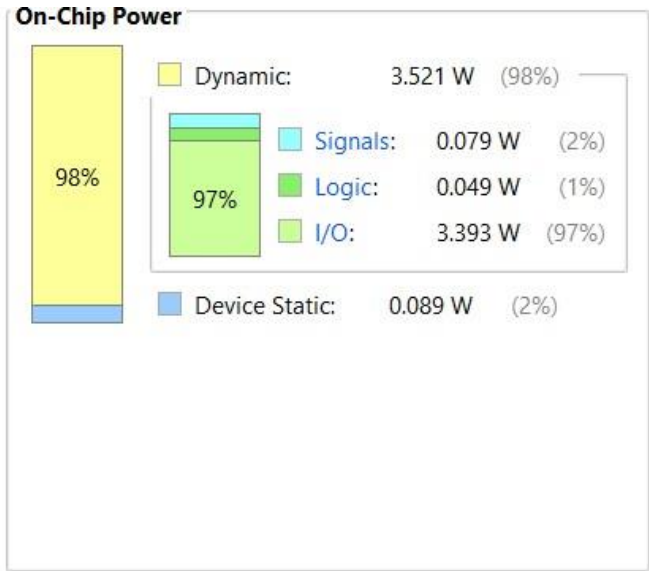[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



8. 4-Bit carry lookahead adder

Verilog code:

```
`timescale 1ns / 1ps

module carry_lookahead_adder_4bit(
    input [3:0] A, B,
    input Cin,
    output [3:0] S,
    output Cout
);
    wire [3:0] Ci;

    assign Ci[0] = Cin;
    assign Ci[1] = (A[0] & B[0]) | ((A[0]^B[0]) & Ci[0]);
    assign Ci[2] = (A[1] & B[1]) | ((A[1]^B[1]) & ((A[0] & B[0]) | ((A[0]^B[0]) & Ci[0])));
    assign Ci[3] = (A[2] & B[2]) | ((A[2]^B[2]) & ((A[1] & B[1]) | ((A[1]^B[1]) & ((A[0] & B[0]) | ((A[0]^B[0]) & Ci[0])))));
    assign Cout = (A[3] & B[3]) | ((A[3]^B[3]) & ((A[2] & B[2]) | ((A[2]^B[2]) & ((A[1] & B[1]) | ((A[1]^B[1]) & ((A[0] & B[0]) | ((A[0]^B[0]) & Ci[0]))))));

    assign S = A^B^Ci;
endmodule
```

Testbench:

```
`timescale 1ns / 1ps


module carry_lookahead_adder_4bit_tb(

);
    reg [3:0] A, B;
    reg Cin;
    wire [3:0] S;
    wire Cout;
    wire[4:0] add;


    carry_lookahead_adder_4bit uut(A, B, Cin, S, Cout);

    assign add = {Cout, S};
    initial begin
        $monitor("A = %b: B = %b, Cin = %b --> S = %b, Cout = %b, Addition = %0d", A, B, Cin, S, Cout, add);
        A = 1; B = 0; Cin = 0; #3;
        A = 2; B = 4; Cin = 1; #3;
        A = 4'hb; B = 4'h6; Cin = 0; #3;
        A = 5; B = 3; Cin = 1;
    end
endmodule
```

Simulation:

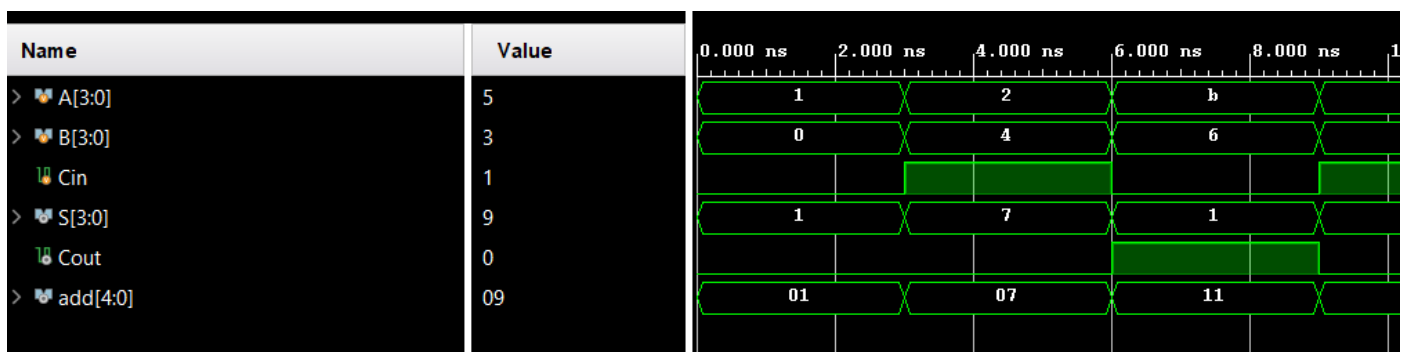

Schematic:

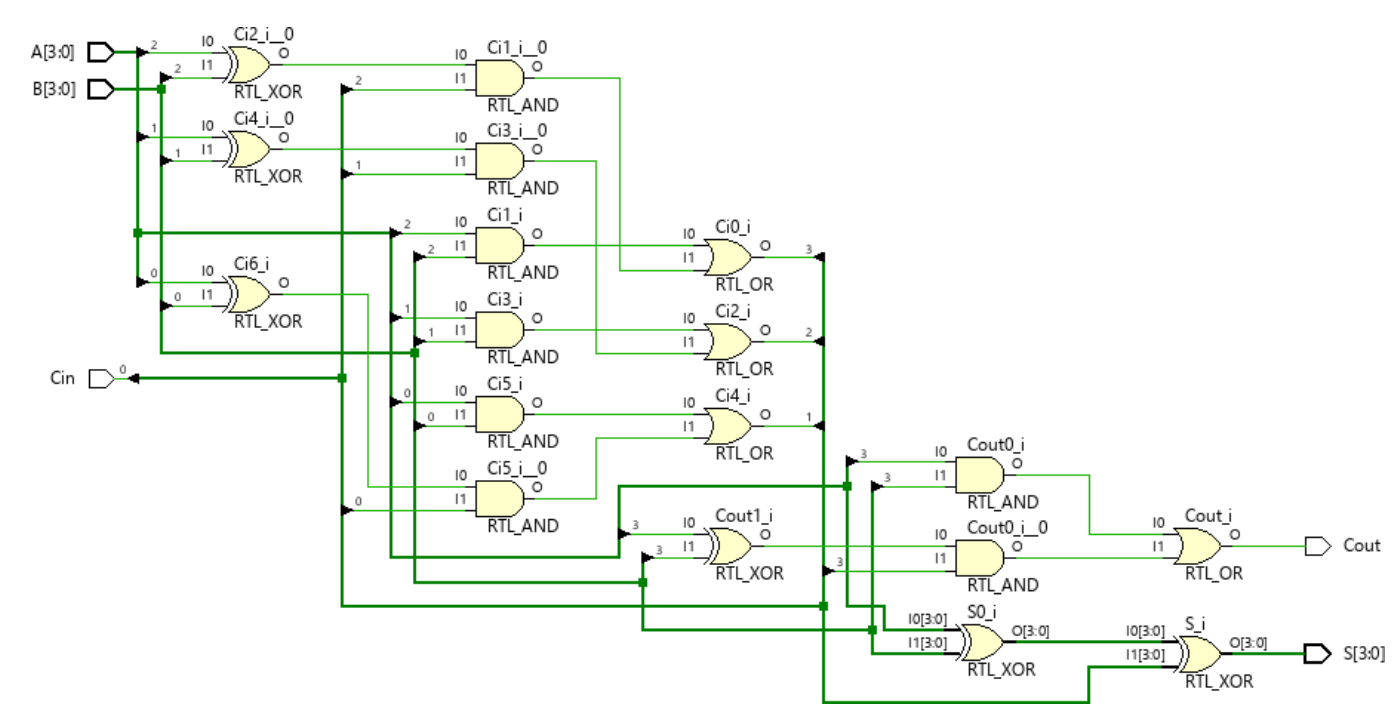

Synthesis report:

Start Writing Synthesis Report

Report BlackBoxes:

+-----+-----+		
BlackBox name Instances		
+-----+-----+		
+-----+-----+		

Report Cell Usage:

+-----+-----+		
Cell Count		
+-----+-----+		
1	LUT3	2
2	LUT5	4
3	IBUF	9
4	OBUF	5
+-----+-----+		

Report Instance Areas:

+-----+-----+-----+			
Instance Module Cells			
+-----+-----+-----+			
1	top		20
+-----+-----+-----+			


Finished Writing Synthesis Report

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	2.954 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.6°C
Thermal Margin:	54.4°C (28.7 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

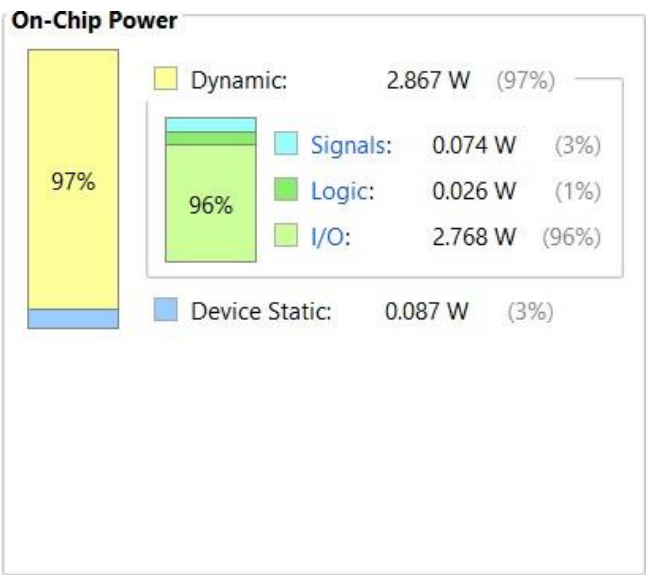[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



9. N-Bit Comparator

Verilog code:

```
`timescale 1ns / 1ps

module n_bit_comparator(
    input [n-1:0] a,
    input [n-1:0] b,
    output reg greater,
    output reg equal,
    output reg lesser
);
    parameter n=3 ;
    always @ (a,b)
    begin

        if(a>b)
        begin
            greater = 1;
            equal   = 0;
            lesser  = 0;
        end

        else if(a==b)
        begin
            greater = 0;
            equal   = 1;
            lesser  = 0;
        end

        else if(a<b)
        begin
            greater = 0;
            equal   = 0;
            lesser  = 1;
        end

    end
endmodule
```

Testbench:

```
timescale 1ns / 1ps

module n_bit_comparator_tb(

);
parameter n=3;
reg [(n-1):0]a;
reg[(n-1):0]b;
wire greater,equal,lesser;

n_bit_comparator uut(a,b,greater,equal,lesser);

initial begin

#10 a=3'b000; b=3'b111;
#10 a=3'b001; b=3'b000;
#10 a=3'b101; b=3'b101;
#10 a=3'b011; b=3'b100;
#10 a=3'b010; b=3'b010;
#10 a=3'b111; b=3'b111;
#10 $finish;

end


initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0);

end
endmodule
```

Simulation:

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns	50.000 ns	60.000 ns
> a[2:0]	7	x	0	1	5	3	2	7
> b[2:0]	7	x	7	0	5	4	2	7
greater	0							
equal	1							
lesser	0							
> n[31:0]	00000003	00000003						

Schematic:

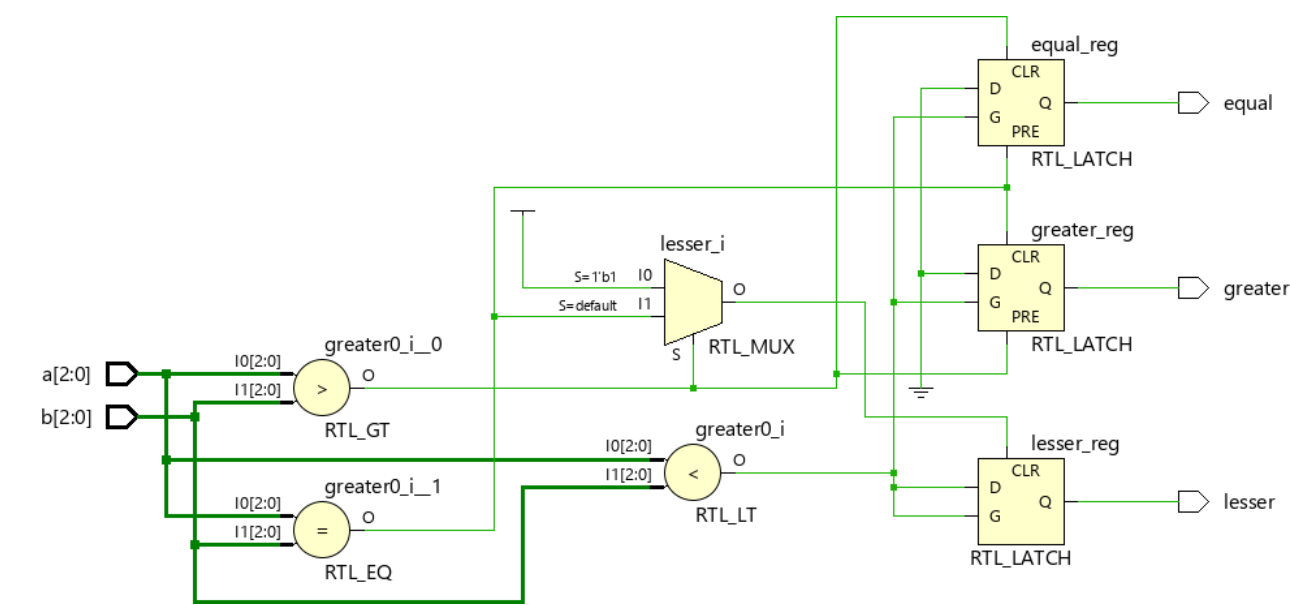

Synthesis report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
++-----++
| |BlackBox name |Instances |
++-----++
++-----++

Report Cell Usage:
+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |LUT6 |    5|
|2      |LDC  |    1|
|3      |LDCP |    2|
|4      |IBUF |    6|
|5      |OBUF |    3|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+
|1      |top      |      |    17|
+-----+-----+-----+
-----


Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.341 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	25.6°C
Thermal Margin:	59.4°C (31.3 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

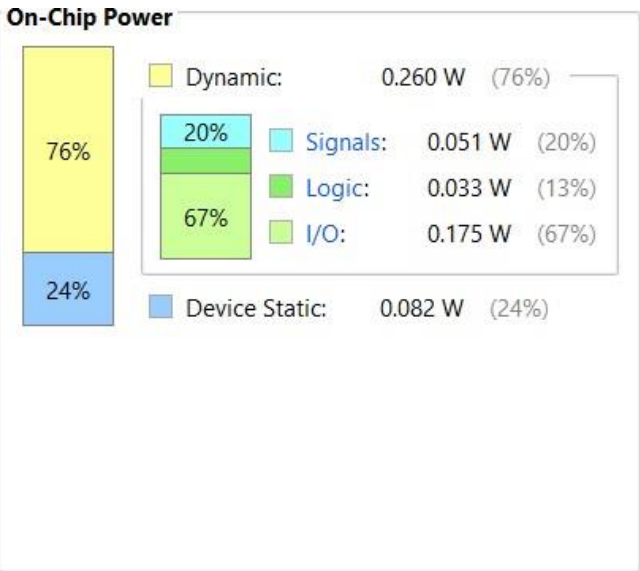[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



10. Serial in serial out shift register

Verilog code:

```
`timescale 1ns / 1ps

module serial_in_serial_out(
    input clk,
    input rst,
    output reg [3:0] q,
    input s_in,
    output reg s_out
);

    always @ (posedge clk)
    begin
        if(rst)
        begin
            q=4'b0000;
            s_out=1'b0;
        end
        else
        begin
            q=q<<1;
            q[0]=s_in;
            s_out = q[3];
        end
    end
endmodule
```

Testbench:

```

`timescale 1ns / 1ps

module serial_in_serial_out_tb(

);

    reg clk,s_in;
    reg rst;
    wire [3:0]q;
    wire s_out;

    serial_in_serial_out uut(clk,rst,q,s_in,s_out);


    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end
    initial
        begin
            #10 rst = 1'b1;
            #10 rst = 1'b0;
            #100 $finish;

        end
    initial begin


        #10 s_in = 1'b0;
        #10 s_in = 1'b1;
        #10 s_in = 1'b1;
        #10 s_in = 1'b0;
        #10 s_in = 1'b1;
        #10 s_in = 1'b0;
        #10 s_in = 1'b1;
        #10 $finish;
    end
endmodule

```

Simulation:

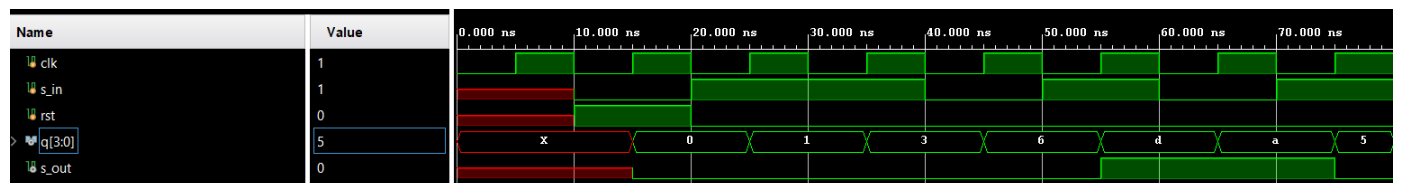

Schematic:

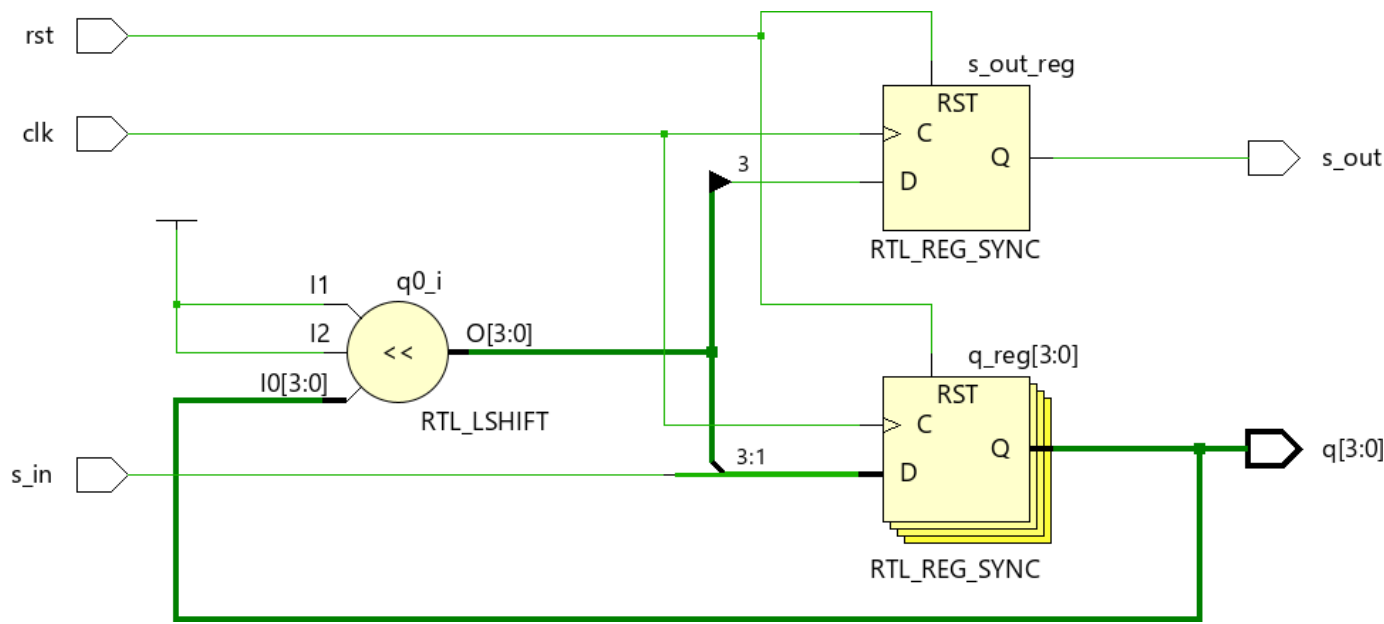

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |BUFG |    1|
|2      |LUT2 |    2|
|3      |FDRE |    4|
|4      |IBUF |    3|
|5      |OBUF |    5|
+-----+-----+-----+

Report Instance Areas:
+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+
|1      |top      |      |    15|
+-----+-----+-----+
-----

Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.32 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 27.5°C


Thermal Margin: 57.5°C (30.3 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

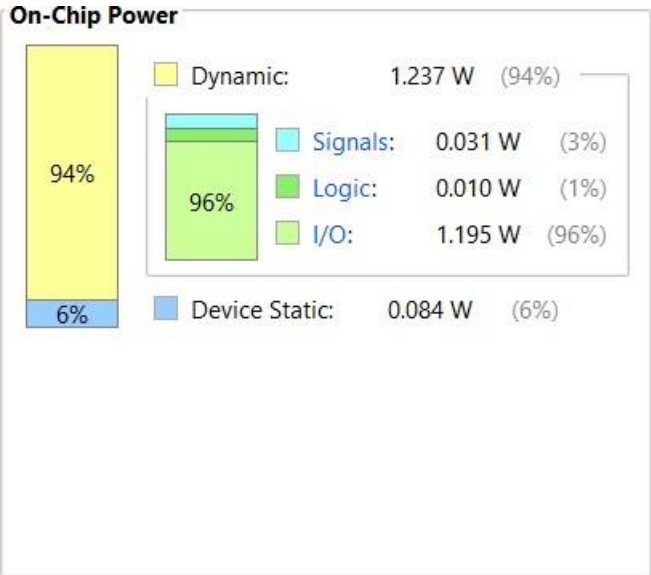[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



11. Serial in parallel out shift register

Verilog code:

```
`timescale 1ns / 1ps

module serial_in_parallel_out(
    input clk,
    input rst,
    input s_in,
    output [3:0] s_out
);
    Dff d1(clk,reset,s_in,s_out[0]);
    Dff d2(clk,reset,s_out[0],s_out[1]);
    Dff d3(clk,reset,s_out[1],s_out[2]);
    Dff d4(clk,reset,s_out[2],s_out[3]);
endmodule

module Dff(
    input clk,
    input rst,
    input d,
    output reg q
);
    always @ (posedge clk)
    begin
        if(rst)
            q=0;

        else if(clk)

            q = d ;
    end
endmodule
```

Testbench:

```

module serial_in_parallel_out_tb(

);
reg clk,rst;
reg s_in;
wire [3:0]s_out;

serial_in_parallel_out uut(clk,rst,s_in,s_out);

initial begin

clk = 1'b0;
forever #5 clk = ~clk;
end

initial begin
rst=1'b1;

#10 rst = 1'b0;

end

always @ (posedge clk,s_in)
begin


#10 s_in = 1'b0;
#10 s_in = 1'b1;
#10 s_in = 1'b1;
#10 s_in = 1'b0;
#10 s_in = 1'b1;
#10 s_in = 1'b0;
#10 s_in = 1'b1;
#10 $finish;

end


endmodule

```

Simulation:

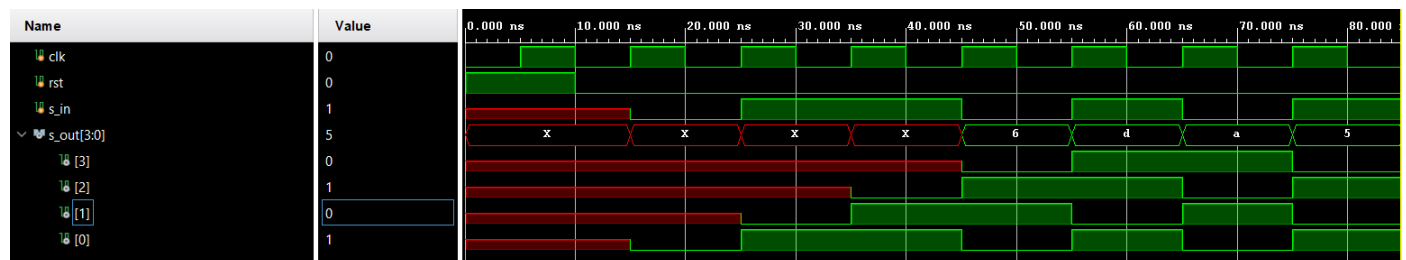

Schematic:

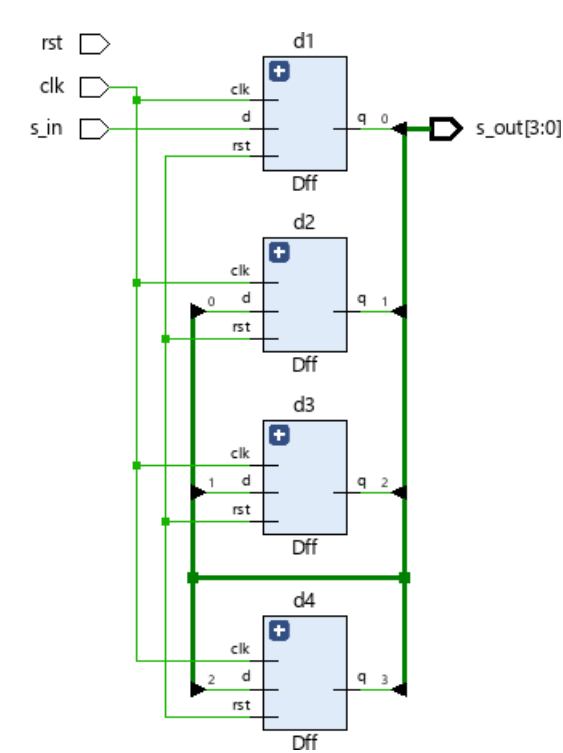

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+
| |BlackBox name |Instances |
+-+-----+
+-+-----+

Report Cell Usage:
+-----+-----+-----+
|         |Cell |Count |
+-----+-----+-----+
|1        |BUFG |    1|
|2        |FDRE |    4|
|3        |IBUF |    2|
|4        |OBUF |    4|
+-----+-----+-----+

Report Instance Areas:
+-+-----+-----+-----+
|         |Instance |Module |Cells |
+-+-----+-----+-----+
|1        |top      |       |    11|
|2        | d1      |Dff    |     1|
|3        | d2      |Dff_0  |     1|
|4        | d3      |Dff_1  |     1|
|5        | d4      |Dff_2  |     1|
+-----+-----+-----+
-----
Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.075 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 27.0°C


Thermal Margin: 58.0°C (30.6 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

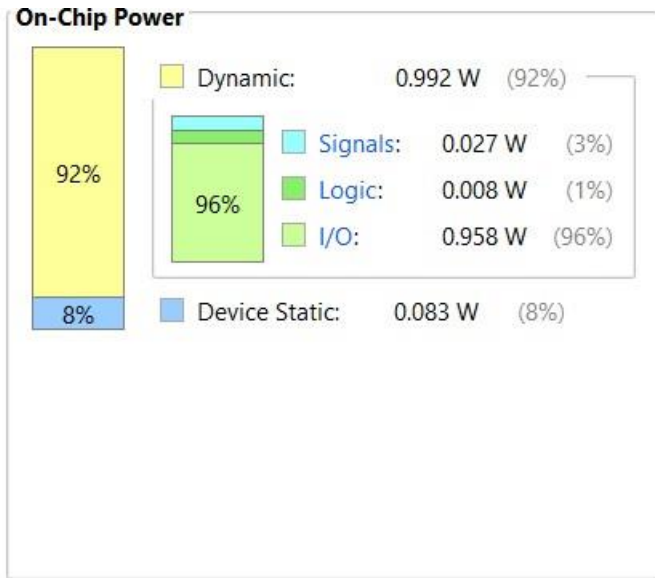[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



12.Parallel in parallel out register

Verilog code:

```
module parallel_in_parallel_out(
    input clk,
    input rst,
    input [3:0] d,
    output reg [3:0] q
);
    always @ (posedge clk,d)
    begin
        if(rst)
            q<=4'b0000;
        else
            q<=d;
    end
endmodule
```

Testbench:

```
module parallel_in_parallel_out_tb(
    );
    reg clk,rst;
    reg [3:0]d;
    wire [3:0]q;

    parallel_in_parallel_out uut(clk,rst,d,q);


    initial begin
        $monitor("%t | d = %b | q = %b",$time,d,q);
    end

    initial begin
        clk=1'b0;
        forever #5 clk=~clk;
    end


    initial begin
        rst = 1'b1;
        #10 rst = 1'b0;
    end

    initial begin
        #00 d=4'b0000;
        #10 d=4'b1001;
        #10 d=4'b1011;
        #10 d=4'b1101;
        #10 d=4'b0101;rst=1'b1;
        #10 d=4'b1010;rst=1'b0;
        #10 d=4'b1100;
        #10 d=4'b1111;
        #10 $finish;
    end
endmodule
```

Simulation:

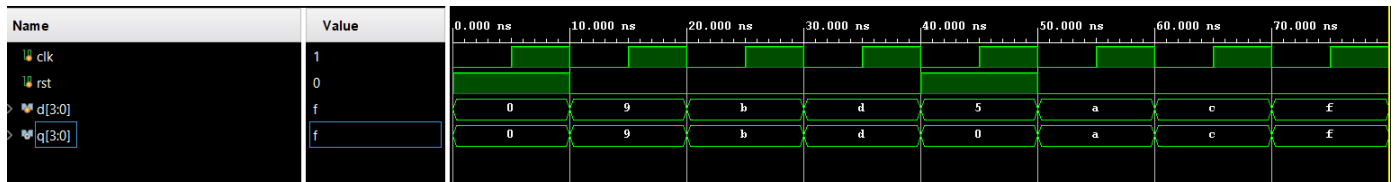

Schematic:

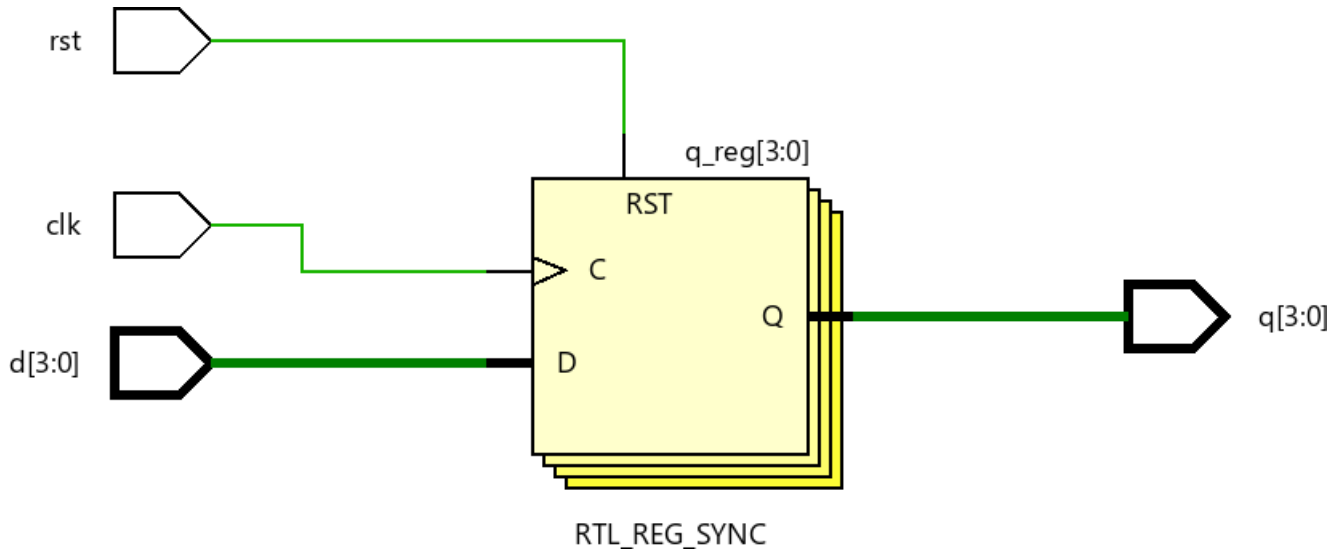

Synthesis report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
1 BUFG	1
2 FDRE	4
3 IBUF	6
4 OBUF	4

Report Instance Areas:

Instance	Module	Cells
1 top		15


Finished Writing Synthesis Report

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	1.093 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	27.1°C
Thermal Margin:	57.9°C (30.6 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

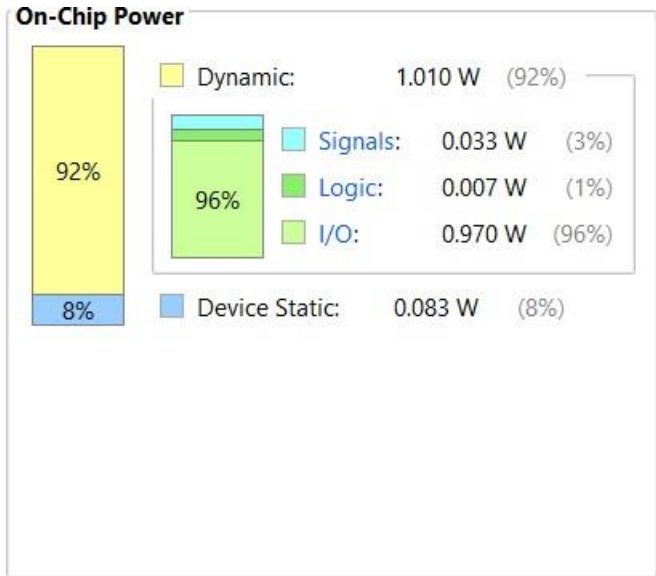[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



13.Parallel in serial out register

Verilog code:

```
module parallel_in_serial_out(
    input clk,ld,rst,[3:0] d,
    output out,
    output [3:0]q
);
    wire x1,x2,x3;

    d_ff d1(clk,rst,d[0],x1);
    logic s1(d[1],x1,ld,q[0]);

    d_ff d2(clk,rst,q[0],x2);
    logic s2(d[2],x2,ld,q[1]);

    d_ff d3(clk,rst,q[1],x3);
    logic s3(d[3],x3,ld,q[2]);

    d_ff d4(clk,rst,q[2],out);
endmodule

module d_ff(
    input clk, rst,d,
    output reg q
);

always @ (posedge clk)
    begin
        if(rst)
            q = 1'b0;
        else
            q = d;
        end
endmodule

module logic(
    input d,si,ld,
    output q
);

assign q = (si & ld) | (d & ~ld);
endmodule
```


Testbench:

```

module parallel_in_serial_out_tb(
);
reg clk,ld;
reg rst;
reg [3:0]d;
wire out;

parallel_in_serial_out uut(clk,ld,rst,d,out);

    initial begin
        clk = 1'b0;
        forever #5 clk = ~clk;
    end

    initial begin
        rst = 1'b1; ld = 1'b1;
        #10 rst = 1'b0; ld = 1'b0;
    end


    initial begin
        #00 d=4'b0000;
        #10 d=4'b1001;
        #10 d=4'b1011;
        #10 d=4'b1101;
        #10 d=4'b0101;
        #10 d=4'b1010;
        #10 d=4'b1100;
        #10 d=4'b1111;

        #10 $finish;
    end


endmodule

```

Simulation:

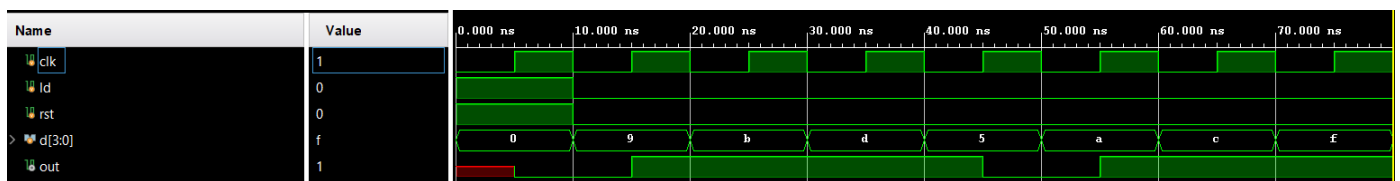

Schematic:

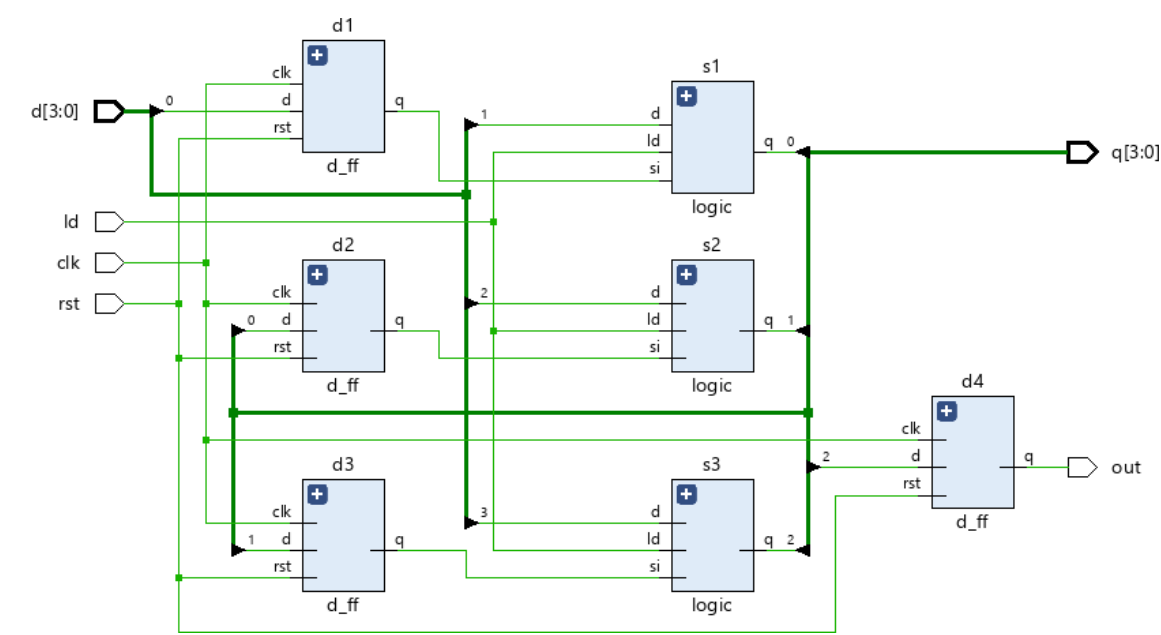

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| BUFG | 1|
|2| LUT3 | 3|
|3| LUT4 | 2|
|4| FDRE | 4|
|5| IBUF | 7|
|6| OBUF | 4|
|7| OBUFT | 1|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1| top | | 22|
|2| d1 |d_ff | 2|
|3| d2 |d_ff_0 | 2|
|4| d3 |d_ff_1 | 1|
|5| d4 |d_ff_2 | 1|
|6| s1 |logic | 1|
|7| s2 |logic_3 | 1|
|8| s3 |logic_4 | 1|
+-----+

Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.636 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 28.1°C


Thermal Margin: 56.9°C (30.0 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

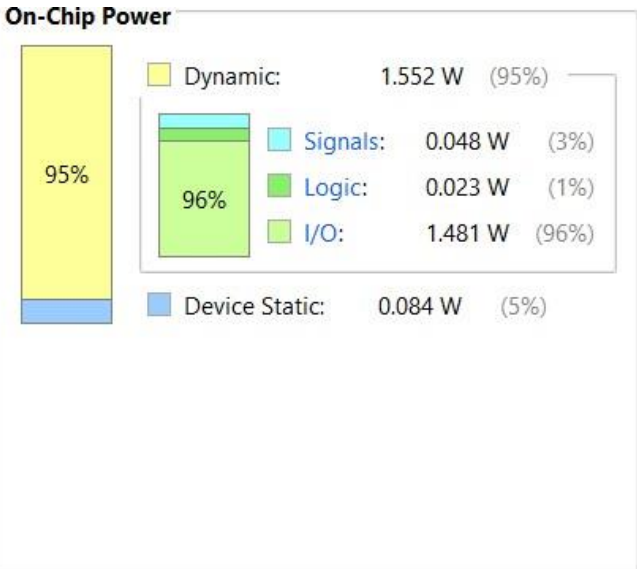[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



14. Bidirection shift register

Verilog code:

```
module bidirection_shift_register(
input clk,rst,dir,d,
output reg [n-1:0]q,
output reg out
);
parameter n = 4;

always @ (posedge clk)
begin

    if(rst)
        q = 4'b0000;
    else
        begin
            case(dir)
                0 : begin q = {q[n-2:0],d}; out <= q[0]; end
                1 : begin q = {d,q[n-1:1]}; out <= q[0]; end
            endcase
        end

    end
endmodule
```

Testbench:

```
module bidirection_shift_register_tb( );
parameter n = 4;
reg clk,rst,dir,d;
wire [n-1:0]q;
wire out;

    bidirection_shift_register uut(clk,rst,dir,d,q,out );

    initial begin
        $monitor("clk = %t | dir = %b | d = %b | q = %b", $time, dir, d, q);
    end

    initial begin
        clk = 1'b0;
        forever #5 clk = ~clk;
    end


    initial begin
        #10 rst = 1'b1;
        #10 rst = 1'b0;
    end

    initial begin


        #10 dir = 0 ; d=1'b0;
        #10 dir = 0 ; d=1'b1;
        #10 dir = 0 ; d=1'b1;
        #10 dir = 0 ; d=1'b0;
        #10 dir = 0 ; d=1'b1;
        #10 dir = 1 ; d=1'b0;
        #10 dir = 1 ; d=1'b1;
        #10 dir = 1 ; d=1'b1;
        #10 dir = 1 ; d=1'b0;
        #10 dir = 1 ; d=1'b1;

    end
endmodule
```

Simulation:

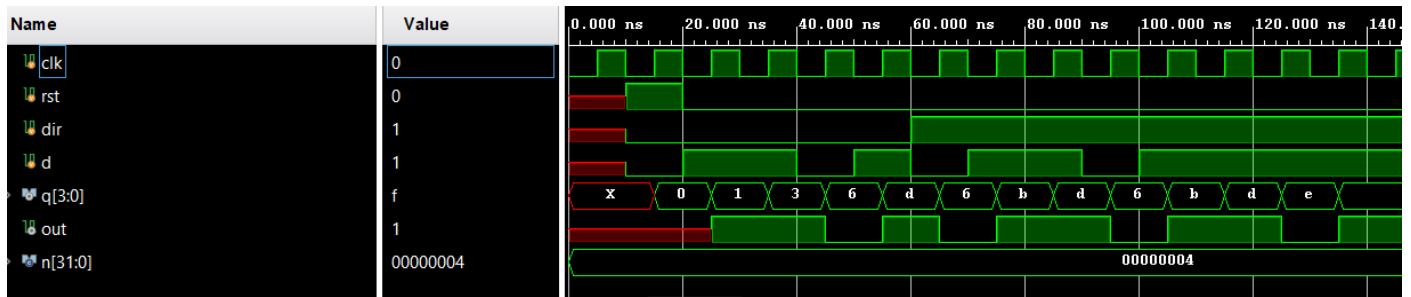

Schematic:

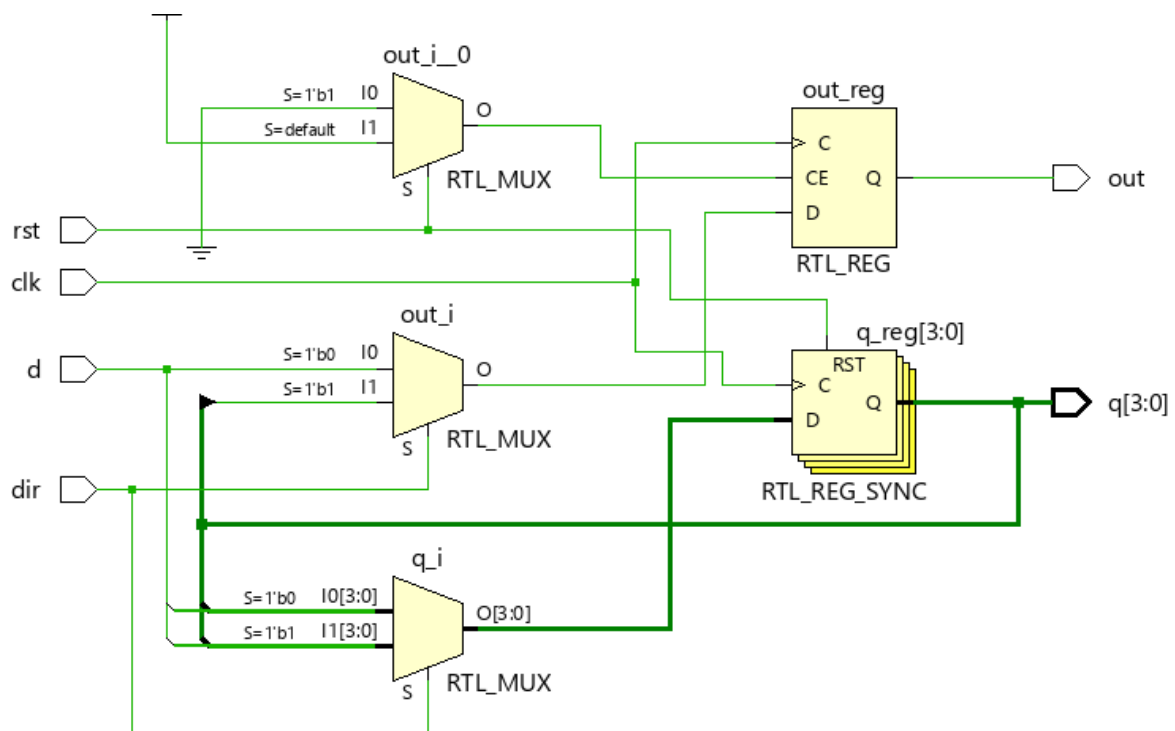

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+++++
| |BlackBox name |Instances |
+++++
+++++

Report Cell Usage:
+++++
|      |Cell |Count |
+++++
|1      |BUFG |    1|
|2      |LUT1 |    1|
|3      |LUT3 |    5|
|4      |FDRE |    5|
|5      |IBUF |    4|
|6      |OBUF |    5|
+++++

Report Instance Areas:
+++++
|      |Instance |Module |Cells |
+++++
|1      |top      |      |    21|
+++++


Finished Writing Synthesis Report
|
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	2.716 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.1°C
Thermal Margin:	54.9°C (28.9 W)
Effective θ JA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

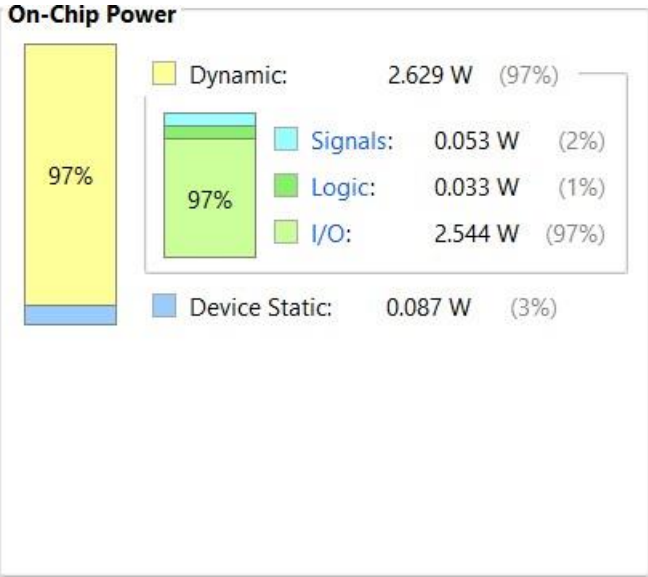[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



15.PRBS Sequence generator


Verilog code:

```
module prbs(  
    input clk,  
    input rst,  
    output out  
);  
    reg [3:0] temp;  
  
    always @ (posedge clk or posedge rst)  
    begin  
        if(rst)  
            temp =4'b1000;  
        else if(clk)  
  
            temp <={temp[1] ^ temp[0],temp[3],temp[2],temp[1]};  
        end  
        assign out = temp[0];  
    endmodule
```


Testbench:

```
module prbs_tb();  
  
    reg clk, rst;  
    wire out;  
  
    prbs uut ( clk, rst,out);  
  
    initial begin  
        $monitor("clk = %t | rst = %b | out = %b ",$time,rst,out);  
    end  
  
    initial begin  
        clk <= 0;  
        forever #5  clk <= ~clk;  
    end  
  
    initial begin  
        rst = 1;  
        #10  rst = 0;  
    end  
  
    initial begin  
        #500 $finish;  
    end  
endmodule
```

Simulation:

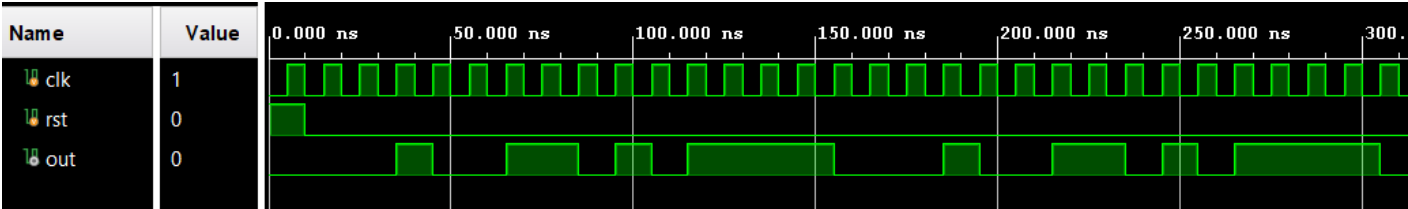

Schematic:

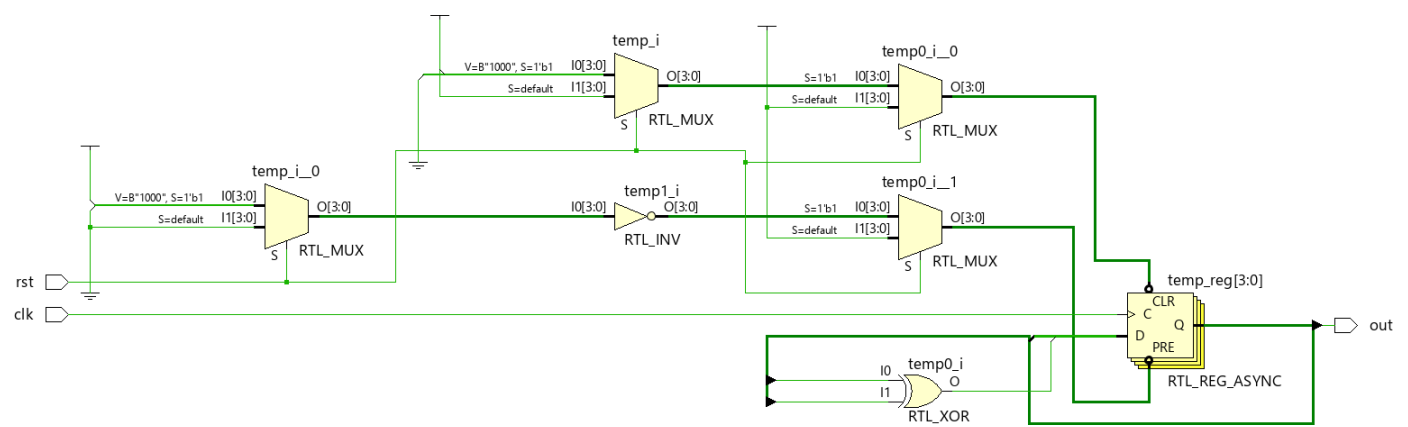

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-+-----+-----+
| |BlackBox name |Instances |
+-+-----+-----+
+-+-----+-----+

Report Cell Usage:
+-----+-----+
|      |Cell |Count |
+-----+-----+
|1      |OBUF |    1|
+-----+-----+


Report Instance Areas:
+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+
|1      |top      |      |    1|
+-----+-----+-----+
-----

Finished Writing Synthesis Report
```


Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.079 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	25.1°C
Thermal Margin:	59.9°C (31.6 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	High
Launch Power Constraint Advisor to find and fix invalid switching activity	

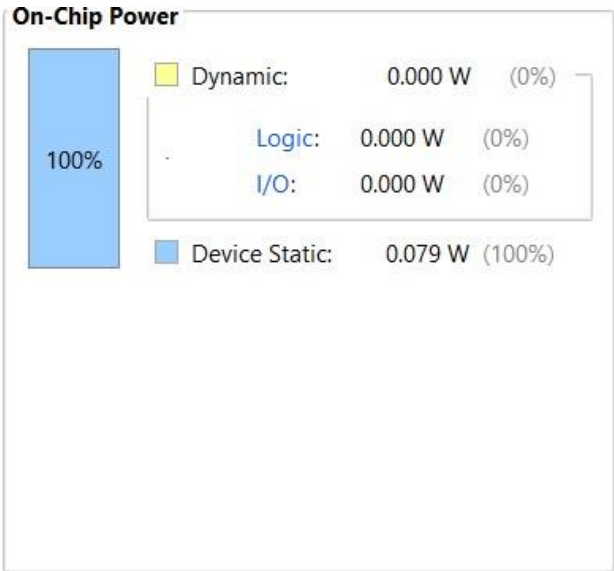

16.8-Bit Subtractor

Verilog code:

```
module subtractor_8bit(
    input [7:0] a, [7:0] b, [7:0] D,
    output Borrow
);
    wire x1,x2,x3,x4,x5,x6,x7;

    full_subtractor s1(a[0],b[0],1'b0,x1,D[0]);
    full_subtractor s2(a[1],b[1],1'b0,x2,D[1]);
    full_subtractor s3(a[2],b[2],1'b0,x3,D[2]);
    full_subtractor s4(a[3],b[3],1'b0,x4,D[3]);
    full_subtractor s5(a[4],b[4],1'b0,x5,D[4]);
    full_subtractor s6(a[5],b[5],1'b0,x6,D[5]);
    full_subtractor s7(a[6],b[6],1'b0,x7,D[6]);
    full_subtractor s8(a[7],b[7],1'b0,Borrow,D[7]);

endmodule

module full_subtractor(
    input x,y,z,
    output borrow,diff
);

    assign diff = x^y^z;
    assign borrow = ~x^y | ~x^z | y^z;

endmodule
```

Testbench:

```
module subtractor_8bit_tb(
);
    reg[7:0]a;
    reg[7:0]b;
    wire [7:0] D;
    wire Borrow;

    initial begin
        $monitor($time | " $time | a = %b | b = %b | borrow = %b | D = %b | borrow = %b ",a,b,Borrow,D);
    end

    subtractor_8bit uut(a,b,D,Borrow);

    initial begin

        #000 a=8'b11000011; b=8'b10000001;
        #100 a=8'b01000011; b=8'b11001001;
        #100 a=8'b11011011; b=8'b10001111;
        #100 a=8'b11110011; b=8'b10100101;
        #100 a=8'b01000011; b=8'b11100001;
        #100 a=8'b00000111; b=8'b10001001;
        #100 a=8'b00100011; b=8'b11000001;
        #100 a=8'b00000011; b=8'b00000001;

        #100 $finish;


    end

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(0);
    end
endmodule
```

Simulation:

Name	Value	0.000 ns	100.000 ns	200.000 ns	300.000 ns	400.000 ns	500.000 ns	600.000 ns	700.000 ns
> a[7:0]	03	c3	43	db	f3	43	07	23	03
> b[7:0]	01	81	c9	8f	a5	e1	89	c1	01
> D[7:0]	02	42	8a	54	56	a2	8e	e2	02
Borrow	1								

Schematic:

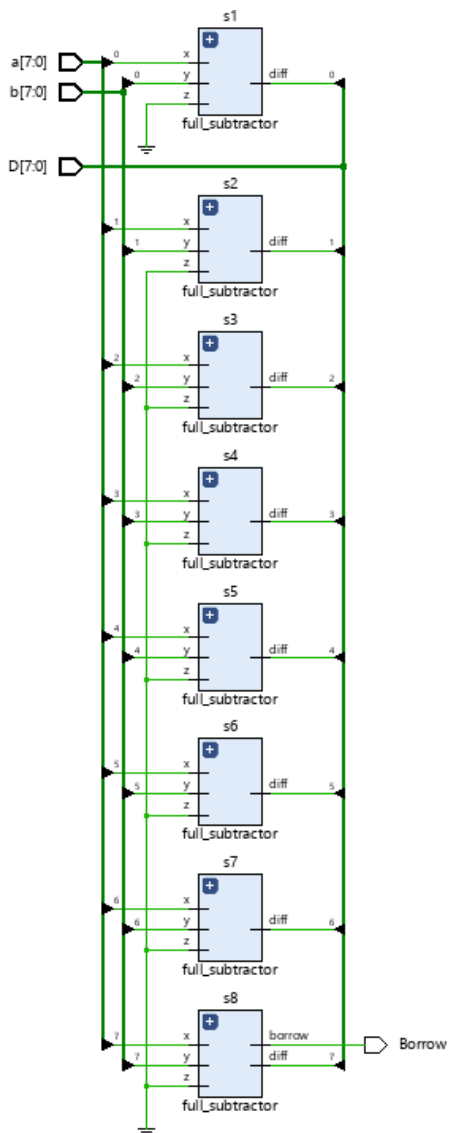

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| BlackBox name |Instances |
+-----+-----+
+-----+-----+

Report Cell Usage:
+-----+-----+
| Cell |Count |
+-----+-----+
|1| LUT2 | 1|
|2| IBUF | 2|
|3| OBUF | 1|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
| Instance |Module |Cells |
+-----+-----+-----+-----+
|1| top | | 4|
+-----+-----+-----+-----+
-----


Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.321 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	25.6°C
Thermal Margin:	59.4°C (31.3 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

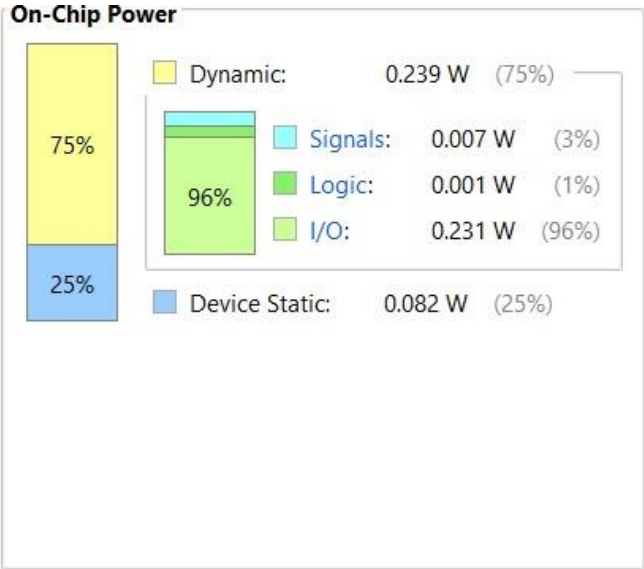[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



17.8-Bit Adder/subtractor

Verilog code:

```
module bit8_adder_sub(
    input [7:0] a,
    input [7:0] b,
    input mode,
    output reg [7:0] result,
    output reg v
);

    reg [7:0] com;

    always @ (a,b,mode)
    begin
        if(mode == 1)
            begin
                com = ~b + 1'b1;
                result = a + com;
                v = (a[7]&com[7]&~result[7]) | (~a[7]&~com[7]&result[7]);
            end
        else if(mode == 0)
            begin
                result = a + b;
                v = (a[7]&b[7]&~result[7]) | (~a[7]&~b[7]&result[7]);
            end
        end
    end

endmodule
```

Testbench:

```
module bit8_sub_add_tb(
);

    reg [7:0] a,b;
    reg mode;
    wire [7:0] result;
    wire v;

    initial begin
        $monitor($time | " $time | a = %b | b = %b | mode = %b | v = %b | result = %b ",a,b,mode,v,result);
    end

    bit8_adder_sub uut(a,b,mode,result,v);

    initial begin
        #000 mode = 1'b1; a=8'b11000011; b=8'b10000001;
        #100 mode = 1'b1; a=8'b01000011; b=8'b11001001;
        #100 mode = 1'b1; a=8'b11011011; b=8'b10001111;
        #100 mode = 1'b1; a=8'b11110011; b=8'b10100101;
        #100 mode = 1'b0; a=8'b01000011; b=8'b11100001;
        #100 mode = 1'b0; a=8'b00000111; b=8'b10001001;
        #100 mode = 1'b0; a=8'b00100011; b=8'b11000001;
        #100 mode = 1'b0; a=8'b00000011; b=8'b00000001;
        #100 $finish;
    end


    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(0);
    end

endmodule
```

Simulation:

Name	Value	0.000 ns	100.000 ns	200.000 ns	300.000 ns	400.000 ns	500.000 ns	600.000 ns	700.000 ns
> a[7:0]	03	c3	43	db	f3	43	07	23	03
> b[7:0]	01	81	c9	8f	a5	e1	89	c1	01
> mode	0								
> result[7:0]	04	42	7a	4c	4e	24	90	e4	04
> v	0								

Schematic:

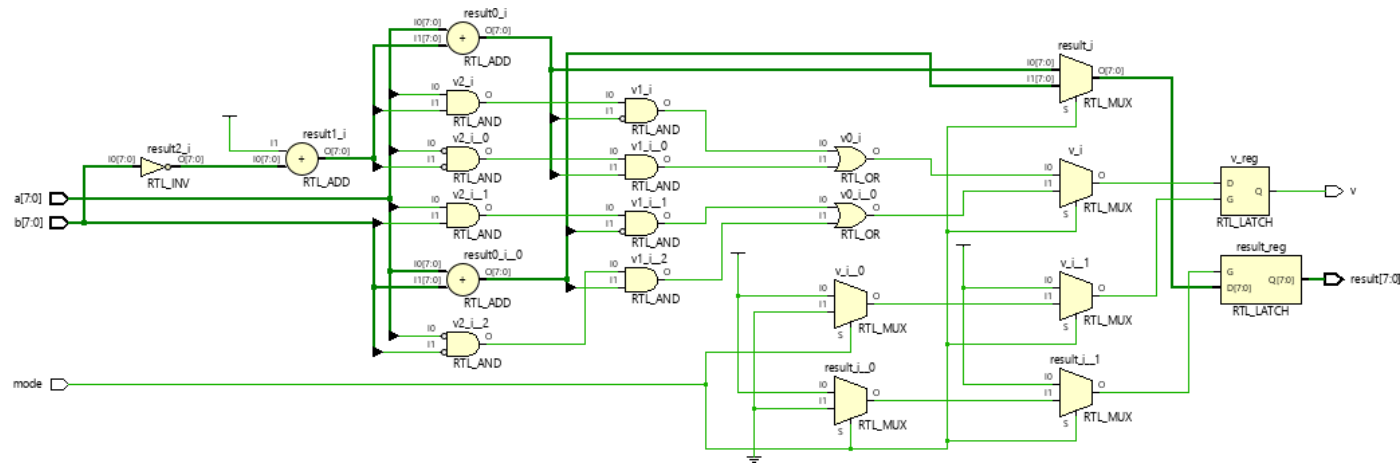

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell      |Count |
+-----+
|1| CARRY4  | 4 |
|2| LUT2    | 16|
|3| LUT3    | 8 |
|4| LUT4    | 2 |
|5| LUT6    | 1 |
|6| IBUF    | 17|
|7| OBUF    | 9 |
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1| top     |      | 57 |
+-----+


Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	6.45 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	37.1°C
Thermal Margin:	47.9°C (25.2 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

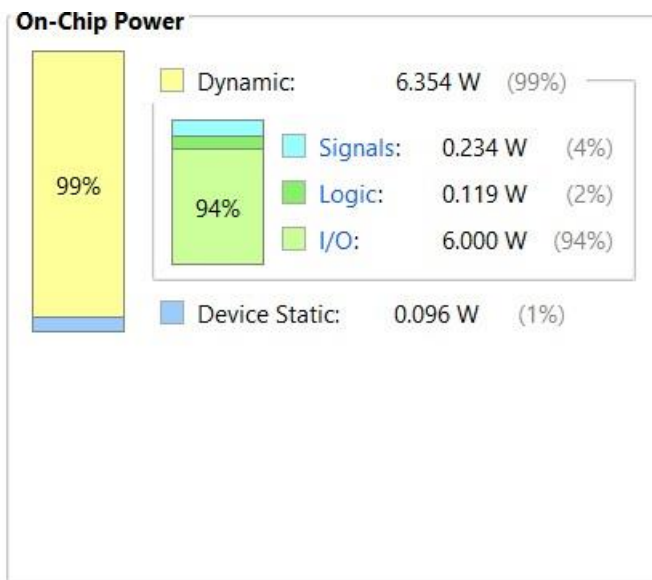[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



18.4-Bit Multiplier

Verilog code:

```
module multiplier_4bit(
    product,inp1,inp2
);
    output [7:0]product;
    input [3:0]inp1;
    input [3:0]inp2;

    assign product[0]=(inp1[0]&inp2[0]);

    wire x1,x2,x3,x4,x5,x6,x7,x8,x9,x10,x11,x12,x13,x14,x15,x16,x17;

    HA HA1(product[1],x1,(inp1[1]&inp2[0]),(inp1[0]&inp2[1]));
    FA FA1(x2,x3,inp1[1]&inp2[1],(inp1[0]&inp2[2]),x1);
    FA FA2(x4,x5,(inp1[1]&inp2[2]),(inp1[0]&inp2[3]),x3);
    HA HA2(x6,x7,(inp1[1]&inp2[3]),x5);

    HA HA3(product[2],x15,x2,(inp1[2]&inp2[0]));
    FA FA5(x14,x16,x4,(inp1[2]&inp2[1]),x15);
    FA FA4(x13,x17,x6,(inp1[2]&inp2[2]),x16);
    FA FA3(x9,x8,x7,(inp1[2]&inp2[3]),x17);

    HA HA4(product[3],x12,x14,(inp1[3]&inp2[0]));
    FA FA8(product[4],x11,x13,(inp1[3]&inp2[1]),x12);
    FA FA7(product[5],x10,x9,(inp1[3]&inp2[2]),x11);
    FA FA6(product[6],product[7],x8,(inp1[3]&inp2[3]),x10);
endmodule

module HA(sout,cout,a,b);
    output sout,cout;
    input a,b;
    assign sout=a^b;
    assign cout=(a&b);
endmodule

module FA(sout,cout,a,b,cin);
    output sout,cout;
    input a,b,cin;
    assign sout=(a^b^cin);
    assign cout=((a&b)|(a&cin)|(b&cin));
endmodule
```


Testbench:

```
module multiplier_4bit_tb(
    );
    reg [3:0]inp1;
    reg [3:0]inp2;
    wire [7:0]product;

    multiplier_4bit uut(.inp1(inp1),.inp2(inp2),.product(product));

    initial
    begin
        inp1=10;
        inp2=12;
        #30 ;

        inp1=13;
        inp2=12;
        #30 ;


        inp1=10;
        inp2=22;
        #30 ;

        inp1=11;
        inp2=22;
        #30 ;


        inp1=12;
        inp2=15;
        #30 ;

        $finish;
    end
endmodule
```

Simulation:

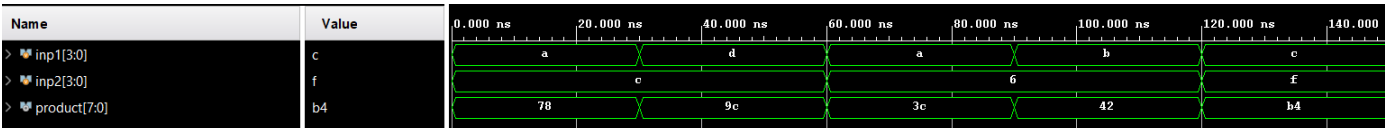

Schematic:

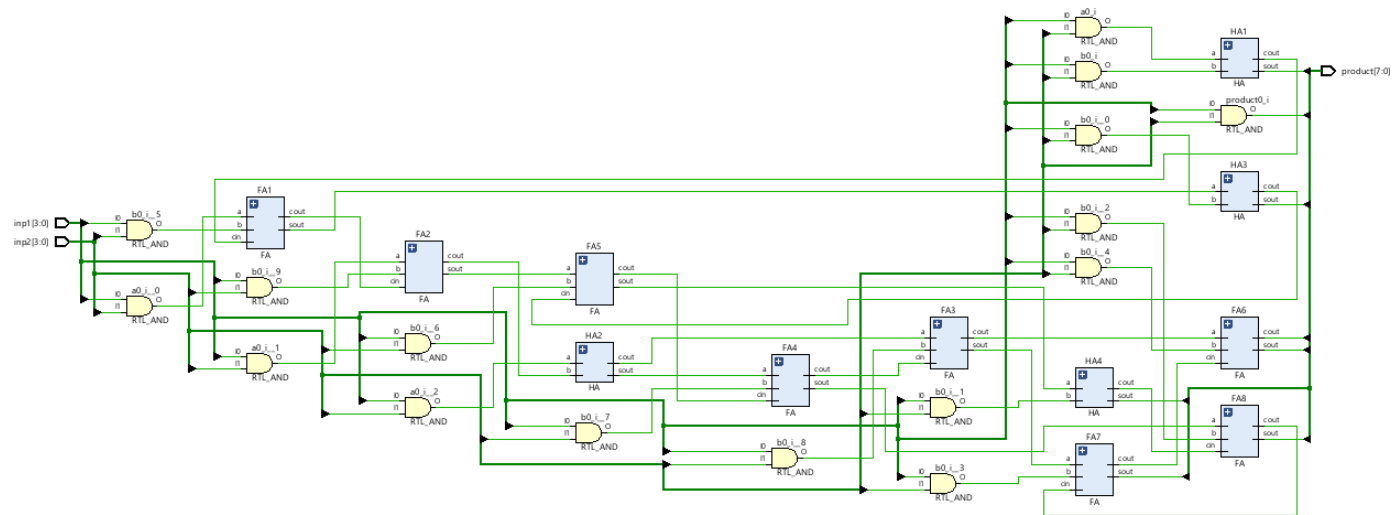

Synthesis report:

Start Writing Synthesis Report

Report BlackBoxes:

+-----+-----+		
BlackBox name Instances		
+-----+-----+		
+-----+-----+		

Report Cell Usage:

+-----+-----+		
Cell Count		
+-----+-----+		
1	LUT2	1
2	LUT4	6
3	LUT6	11
4	IBUF	8
5	OBUF	8
+-----+-----+		

Report Instance Areas:

+-----+-----+-----+			
Instance Module Cells			
+-----+-----+-----+			
1	top		34
+-----+-----+-----+			

Finished Writing Synthesis Report

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 4.135 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 32.8°C


Thermal Margin: 52.2°C (27.5 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

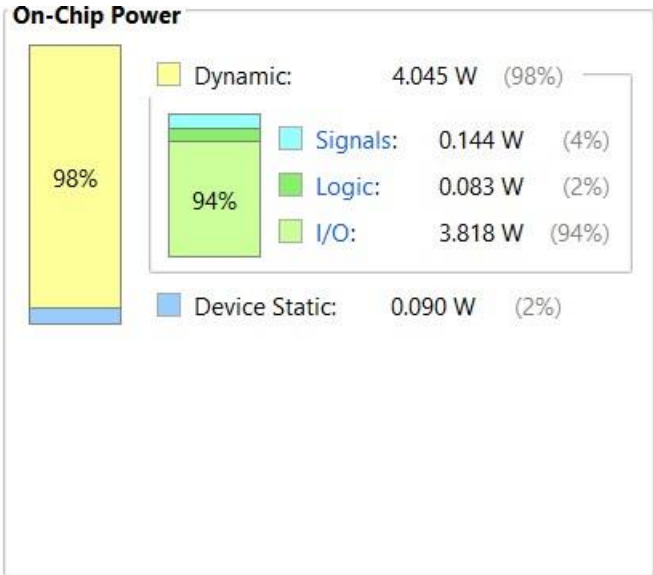[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



19. Fixed point division

Verilog code:

```
module fixed_point_division(divisor, dividend, remainder, result);  
  
input [7:0] divisor, dividend;  
output reg [7:0] result, remainder;  
  
integer i;  
reg [7:0] divisor_copy, dividend_copy;  
reg [7:0] temp;  
  
always @(divisor or dividend)  
begin  
    divisor_copy = divisor;  
    dividend_copy = dividend;  
    temp = 0;  
    for(i = 0; i < 8; i = i + 1)  
    begin  
        temp = {temp[6:0], dividend_copy[7]};  
        dividend_copy[7:1] = dividend_copy[6:0];  
  
        temp = temp - divisor_copy;  
  
        if(temp[7] == 1)  
        begin  
            dividend_copy[0] = 0;  
            temp = temp + divisor_copy;  
        end  
        else  
        begin  
            dividend_copy[0] = 1;  
        end  
    end  
    result = dividend_copy;  
    remainder = dividend - (divisor_copy*dividend_copy);  
end  
endmodule
```

Testbench:

```

module fixed_point_division_tb;

    reg [7:0] divisor;
    reg [7:0] dividend;

    wire [7:0] remainder;
    wire [7:0] result;

    fixed_point_division uut (divisor, dividend, remainder, result);

    initial begin
        divisor = 13;
        dividend = 28;

        #100;

        divisor = 5;
        dividend = 25;

        #100
        divisor = 6;
        dividend = 37;
    end


    initial begin
        $monitor("Divisor: %d, Dividend: %d, Remainder: %d, Result: %d\n", divisor, dividend, remainder, result);
    end
endmodule

```

Simulation:

Name	Value	0.000 ns	100.000 ns	200.000 ns	300.000 ns	400.000 ns	500.000 ns	600.000 ns
> divisor[7:0]	06	0d	05					06
> dividend[7:0]	25	1c	19					25
> remainder[7:0]	01	02	00					01
> result[7:0]	06	02	05					06

Schematic:

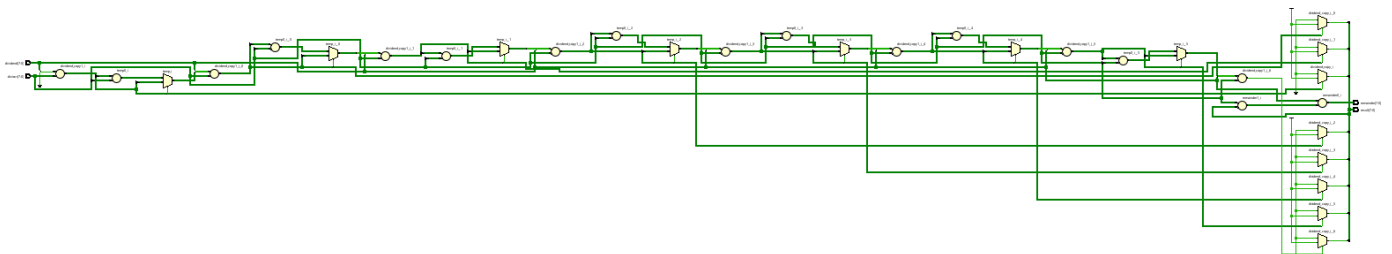

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| |BlackBox name |Instances |
+-----+-----+
+-----+-----+

Report Cell Usage:
+-----+-----+
| |Cell |Count |
+-----+-----+
|1 |CARRY4 | 36 |
|2 |LUT1 | 7 |
|3 |LUT2 | 75 |
|4 |LUT3 | 49 |
|5 |LUT4 | 11 |
|6 |LUT5 | 4 |
|7 |LUT6 | 23 |
|8 |IBUF | 16 |
|9 |OBUF | 16 |
+-----+-----+

Report Instance Areas:
+-----+-----+-----+
| |Instance |Module |Cells |
+-----+-----+-----+
|1 |top | | 237 |
+-----+-----+-----+
-----


Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	17.212 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	57.4°C
Thermal Margin:	27.6°C (14.5 W)
Effective θ JA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

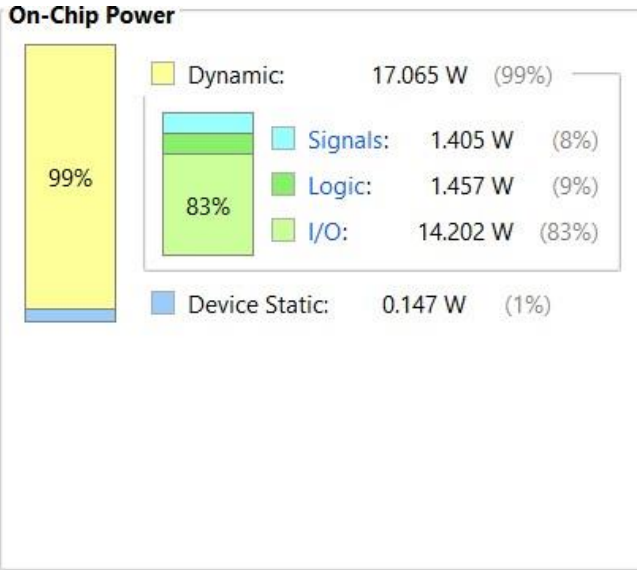[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



20. Master slave JK flip flop

Verilog code:

```
module master_slave_ff(
    input clk,s,r,
    output Q,QBAR
);

    wire w1,w2,w3,w4;
    wire sclk;

    assign sclk = ~clk;

    jk_flipflop master(clk,s,r,w1,w2);
    jk_flipflop slave(sclk,w1,w2,Q,QBAR);
endmodule

module jk_flipflop(
    input clk,
    input j,
    input k,
    output reg q,
    output reg qbar
);

    always @ (posedge clk)
    begin

        case ({j,k})

            2'b00 : begin q <= q; qbar<= ~q; end
            2'b01 : begin q <= 0; qbar<= 1; end
            2'b10 : begin q <= 1; qbar<= 0; end
            2'b11 : begin q <= ~q; qbar<= q; end

        endcase
    end
endmodule
```

Testbench:

```

module master_slave_ff_tb(
    );
    reg clk;
    reg s;
    reg r;
    wire Q;
    wire QBAR;

    master_slave_ff uut (clk,s,r,Q,QBAR);

    initial begin
        $display("Time=%0t clk=%b s=%b r=%b Q=%b QBAR=%b", $time, clk, s, r, Q, QBAR);
    end

    initial begin
        clk=1'b0;
        forever #5 clk=~clk;
    end


    initial begin
        #10 s=1'b0; r=1'b0;
        #10 s=1'b0; r=1'b1;
        #10 s=1'b1; r=1'b0;
        #10 s=1'b1; r=1'b1;
        #10 s=1'b0; r=1'b0;
        #10 s=1'b0; r=1'b1;
        #10 s=1'b1; r=1'b0;
        #10 s=1'b1; r=1'b1;
        #10 $finish;
    end
end
endmodule

```

Simulation:



Schematic:

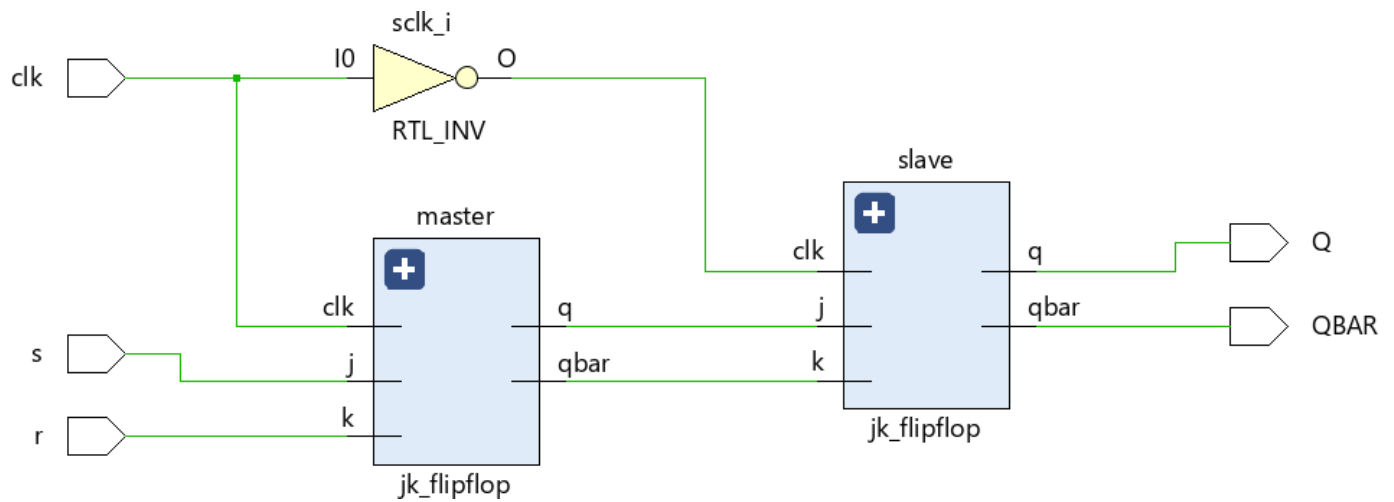

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
| 1 | BUFG | 1 |
| 2 | LUT1 | 1 |
| 3 | LUT3 | 4 |
| 4 | FDRE | 4 |
| 5 | IBUF | 3 |
| 6 | OBUF | 2 |
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
| 1 | top | 15 | |
| 2 | master | jk_flipflop | 5 |
| 3 | slave | jk_flipflop_0 | 3 |
+-----+

Finished Writing Synthesis Report : Time
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.589 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 28.0°C


Thermal Margin: 57.0°C (30.1 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

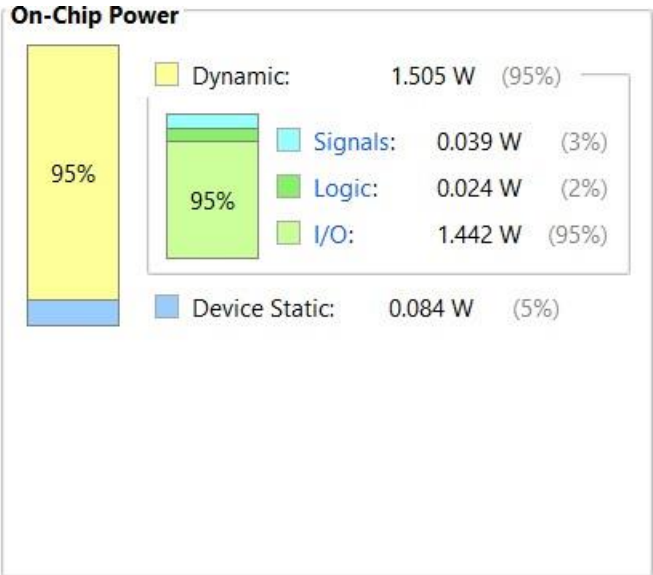[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



21. Positive edge detector

Verilog code:

```
module pos_edge_det (
    input sig,
    input clk,
    output pe
);

    reg sig_dly;

    always @ (posedge clk) begin
        sig_dly <= sig;
    end

    assign pe = sig & ~sig_dly;
endmodule
```


Testbench:

```
module pos_edge_det_tb;
    reg sig;
    reg clk;
    wire pe;
    pos_edge_det uut (sig,clk, pe);


    always #5 clk = ~clk;
    initial begin
        clk <= 0;
        sig <= 0;
        #15 sig <= 1;
        #20 sig <= 0;
        #15 sig <= 1;
        #10 sig <= 0;
        #20 $finish;
    end

    initial begin
        $dumpvars;
        $dumpfile("dump.vcd");
    end
endmodule
```

Simulation:

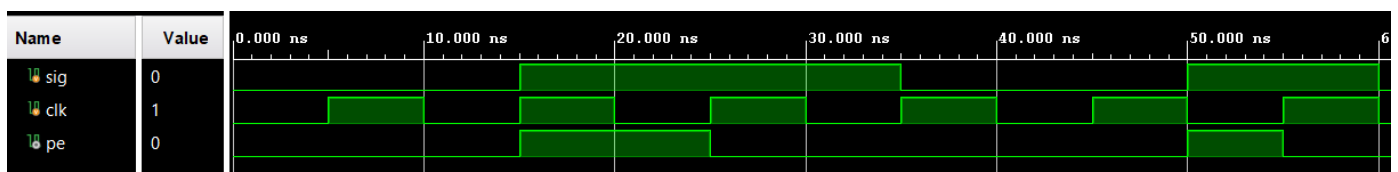

Schematic:

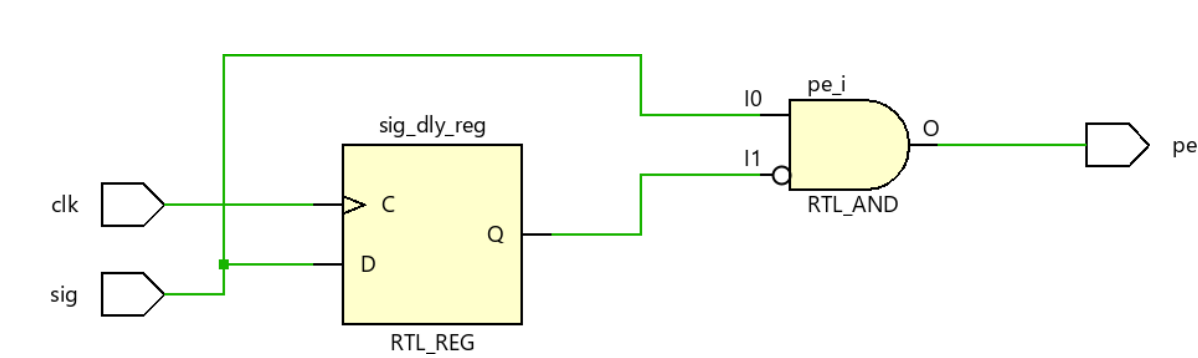

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
| 1 | BUFG | 1 |
| 2 | LUT2 | 1 |
| 3 | FDRE | 1 |
| 4 | IBUF | 2 |
| 5 | OBUF | 1 |
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
| 1 | top | 6 |
+-----+

Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.335 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 25.6°C


Thermal Margin: 59.4°C (31.3 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

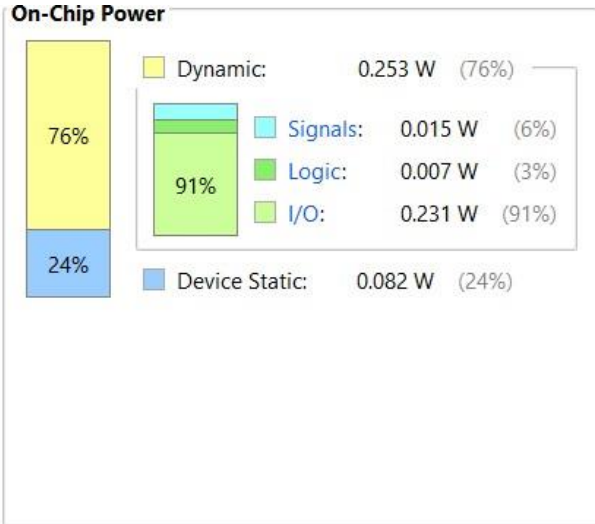[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



22. BCD adder

Verilog code:

```
module bcd_adder(
a,b,carry_in,sum,carry
);
input [3:0] a,b;
input carry_in;
output [3:0] sum;
output carry;

reg [4:0] sum_temp;
reg [3:0] sum;
reg carry;

always @(a,b,carry_in)
begin
    sum_temp = a+b+carry_in;
    if(sum_temp > 9) begin
        sum_temp = sum_temp+6;
        carry = 1;
        sum = sum_temp[3:0];    end
    else begin
        carry = 0;
        sum = sum_temp[3:0];
    end
end
endmodule
```

Testbench:

```
module bcd_adder_tb(
);
    reg [3:0] a;
    reg [3:0] b;
    reg carry_in;


    wire [3:0] sum;
    wire carry;

    bcd_adder uut (
        .a(a),
        .b(b),
        .carry_in(carry_in),
        .sum(sum),
        .carry(carry)
    );


    initial begin

        a = 0; b = 0; carry_in = 0;    #100;
        a = 6; b = 9; carry_in = 0;    #100;
    )    a = 3; b = 3; carry_in = 1;    #100;
    )    a = 4; b = 5; carry_in = 0;    #100;
    )    a = 8; b = 2; carry_in = 0;    #100;
    )    a = 9; b = 9; carry_in = 1;    #100;
    )    end
    ) endmodule
```

Simulation:

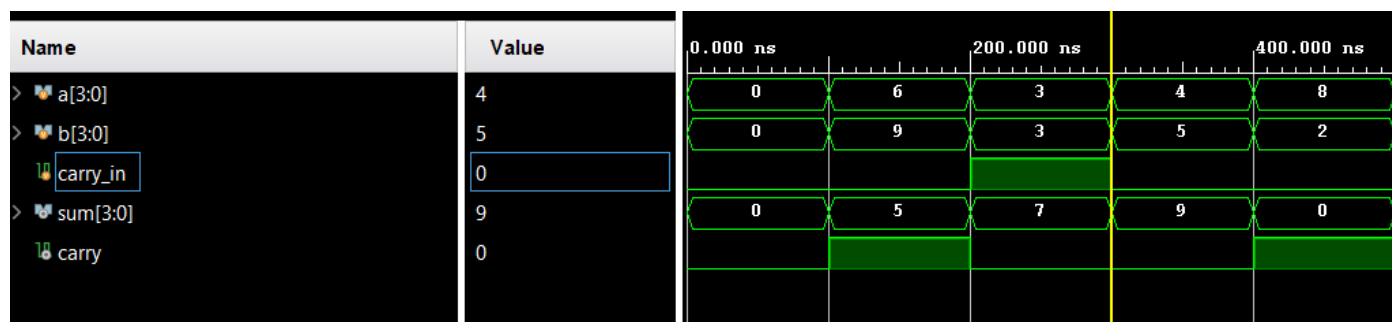

Schematic:

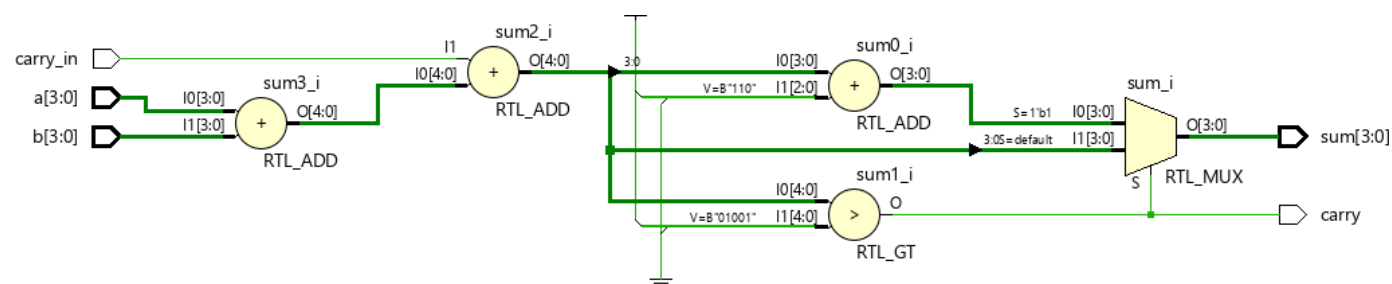

Synthesis report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
LUT3	1
LUT5	2
LUT6	4
IBUF	9
OBUF	5

Report Instance Areas:

Instance	Module	Cells
top		21


Finished Writing Synthesis Report

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	3.133 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.9°C
Thermal Margin:	54.1°C (28.5 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

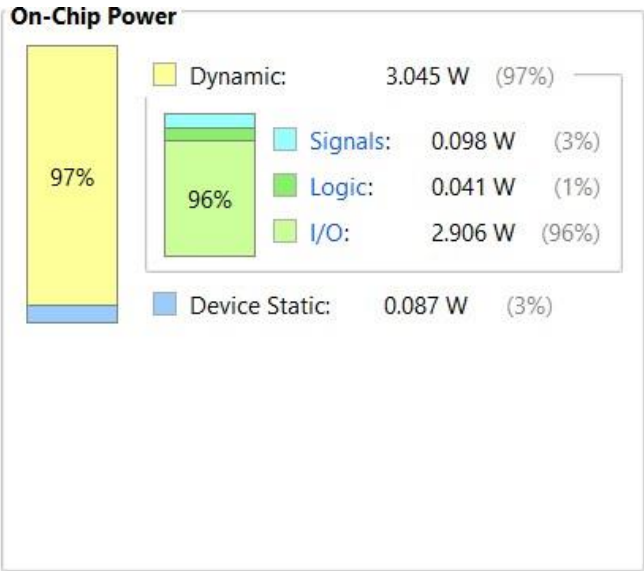[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



23.4-Bit carry select adder

Verilog code:

```
module carry_select_adder
(
    input  [3:0] A,B,
    input  cin,
    output [3:0] S,
    output cout
);

wire [3:0] temp0,temp1,carry0,carry1;

//for carry 0
fulladder fa00(A[0],B[0],1'b0,temp0[0],carry0[0]);
fulladder fa01(A[1],B[1],carry0[0],temp0[1],carry0[1]);
fulladder fa02(A[2],B[2],carry0[1],temp0[2],carry0[2]);
fulladder fa03(A[3],B[3],carry0[2],temp0[3],carry0[3]);

//for carry 1
fulladder fa10(A[0],B[0],1'b1,temp1[0],carry1[0]);
fulladder fa11(A[1],B[1],carry1[0],temp1[1],carry1[1]);
fulladder fa12(A[2],B[2],carry1[1],temp1[2],carry1[2]);
fulladder fa13(A[3],B[3],carry1[2],temp1[3],carry1[3]);

//mux for carry
multiplexer2 mux_carry(carry0[3],carry1[3],cin,cout);
//mux's for sum
multiplexer2 mux_sum0(temp0[0],temp1[0],cin,S[0]);
multiplexer2 mux_sum1(temp0[1],temp1[1],cin,S[1]);
multiplexer2 mux_sum2(temp0[2],temp1[2],cin,S[2]);
multiplexer2 mux_sum3(temp0[3],temp1[3],cin,S[3]);

endmodule
```

Testbench:

```
module fulladder
(
    input a,b,cin,
    output sum,carry
);

assign sum = a ^ b ^ cin;
assign carry = (a & b) | (cin & b) | (a & cin);

endmodule

module multiplexer2
(
    input i0,i1,sel,
    output reg bitout
);


always@(i0,i1,sel)
begin
    if(sel == 0)
        bitout = i0;
    else
        bitout = i1;
    end
end

endmodule
```


Simulation:

Name	Value	0.000 ns	10.000 ns	20.000 ns	30.000 ns	40.000 ns	50.000 ns	60.000 ns	70.000 ns	80.000 ns	90.000 ns	100.000 ns	110.000 ns	120.000 ns	130.000 ns	140.000 ns	150.000 ns
A[3:0]	0	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
B[3:0]	1	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
cin	0	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
S[3:0]	1	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
cout	0	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
i[31:0]	00000000	00000000	00000001	00000002	00000003	00000004	00000005	00000006	00000007	00000008	00000009	0000000a	0000000b	0000000c	0000000d	0000000e	0000000f
j[31:0]	00000001	00000000	00000001	00000002	00000003	00000004	00000005	00000006	00000007	00000008	00000009	0000000a	0000000b	0000000c	0000000d	0000000e	0000000f
error[31:0]	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000	00000000

Schematic:

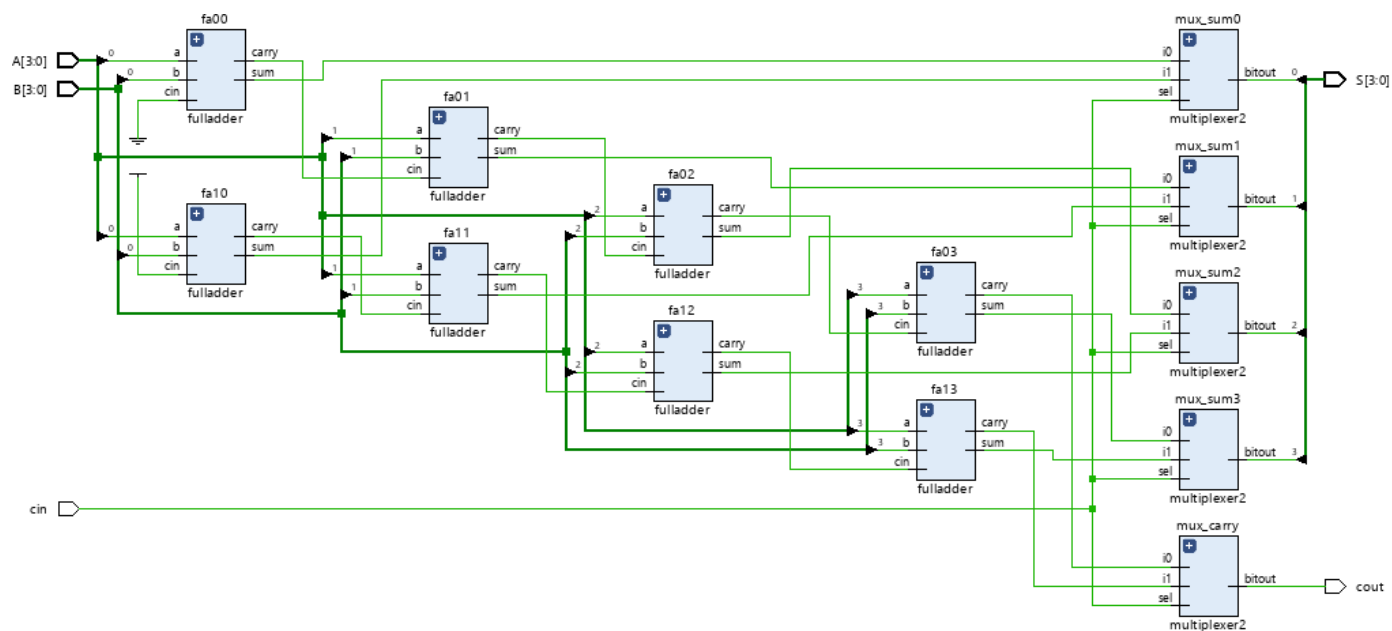

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
++-----+
| |BlackBox name |Instances |
++-----+
++-----+

Report Cell Usage:
+-----+-----+-----+
|      |Cell |Count |
+-----+-----+-----+
|1      |LUT3 |    2|
|2      |LUT5 |    4|
|3      |IBUF |    9|
|4      |OBUF |    5|
+-----+-----+-----+

Report Instance Areas:
+-----+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+-----+
|1      |top      |      |    20|
+-----+-----+-----+-----+
-----


Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	2.956 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.6°C
Thermal Margin:	54.4°C (28.7 W)
Effective θ JA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

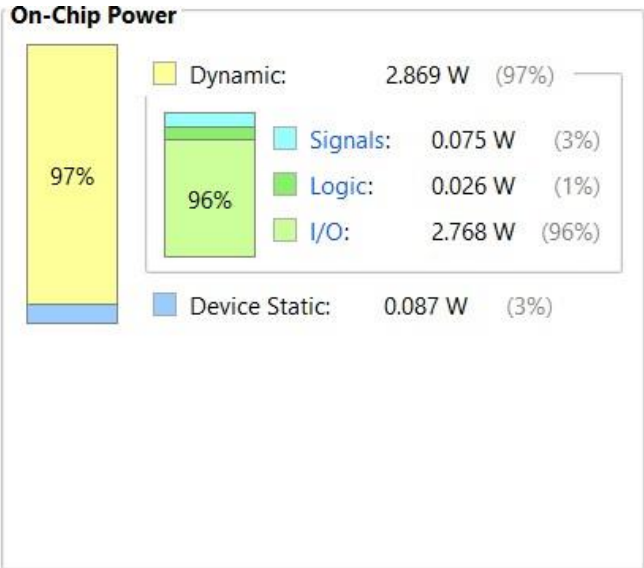[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



24. Moore FSM 1010 sequence detector

Verilog code:

```
module moore_fsm_1010(  
    input clk,  
    input rst,  
    input in,  
    output reg out  
);  
  
    reg [2:0] state, next_state;  
    parameter s0 = 3'b001;  
    parameter s1 = 3'b010;  
    parameter s2 = 3'b011;  
    parameter s3 = 3'b100;  
    parameter s4 = 3'b101;  
  
    always @ (state or in)  
    begin  
        case (state)  
            s0: if (in == 1'b1)  
                begin  
                    next_state = s1;  
                    out=1'b0;  
                end  
            else  
                begin  
                    next_state = s0;  
                    out=1'b0;  
                end  
  
            s1: if (in == 1'b0)  
                begin  
                    next_state = s2;  
                    out=1'b0;  
                end  
            else  
                begin  
                    next_state = s1;  
                    out=1'b0;  
                end  
        endcase  
    end  
endmodule
```

```

s2: if (in == 1'b1)
    begin
        next_state = s3;
        out=1'b0;
    end
    else
        begin
            next_state = s0;
            out=1'b0;
        end
s3: if (in == 1'b0)
    begin
        next_state = s4;
        out=1'b0;
    end
    else
        begin
            next_state = s1;
            out=1'b0;
        end
s4: if (in == 1'b0)
    begin
        next_state = s0;
        out=1'b1;
    end
    else
        begin
            next_state = s1;
            out=1'b1;
        end
    default: next_state = s0;
endcase
end
always@(posedge clk)
    begin
        if (rst)
            state <= s0;
        else
            state <= next_state;
        end
end

```

endmodule

Testbench:

```

module moore_fsm_1010_tb(
);
  reg clk;
  reg rst;
  reg in;
  wire out;


  moore_fsm_1010 uut(clk,rst,in,out);
  initial begin
    $monitor($time," | rst=%b | in=%b | out=%b",rst,in,out );
  end
  initial begin
    clk = 1'b0;
    forever #5 clk = ~clk;
  end

  initial begin
    rst = 1'b1;
    #10 rst = 1'b0; in=1'b0;
    #10 in=1'b1;
    #10 in=1'b0;
    #10 in=1'b1;
    #10 in=1'b1;
    #10 in=1'b0;
    #10 in=1'b1;
    #10 in=1'b0;
    #10 in=1'b1;
    #10 in=1'b0;
    #10 in=1'b0;
  end


  end
endmodule

```

Simulation:

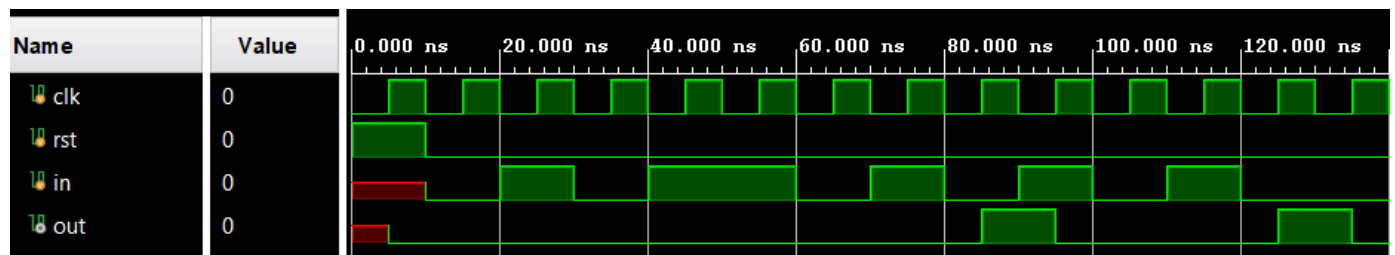

Schematic:

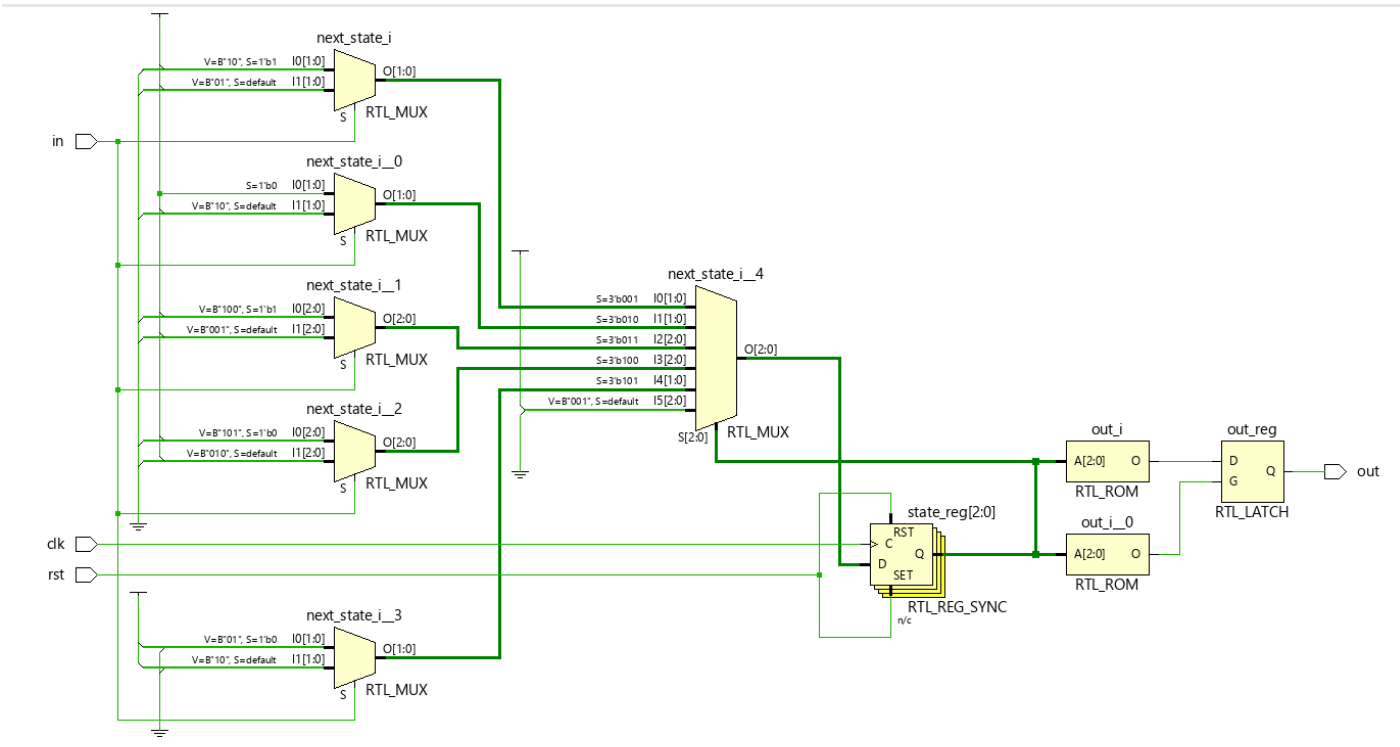

Synthesis report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| BlackBox name |Instances |
+-----+-----+
+-----+-----+

Report Cell Usage:
+-----+-----+
| Cell |Count |
+-----+-----+
|1|BUFG | 1|
|2|LUT2 | 3|
|3|LUT4 | 1|
|4|LUT5 | 2|
|5|FDRE | 4|
|6|FDSE | 1|
|7|LD | 1|
|8|IBUF | 3|
|9|OBUF | 1|
+-----+-----+

Report Instance Areas:
+-----+-----+-----+
| Instance |Module |Cells |
+-----+-----+-----+
|1|top| | 17|
+-----+-----+-----+

Finished Writing Synthesis Report
```

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.126 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 25.2°C


Thermal Margin: 59.8°C (31.5 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

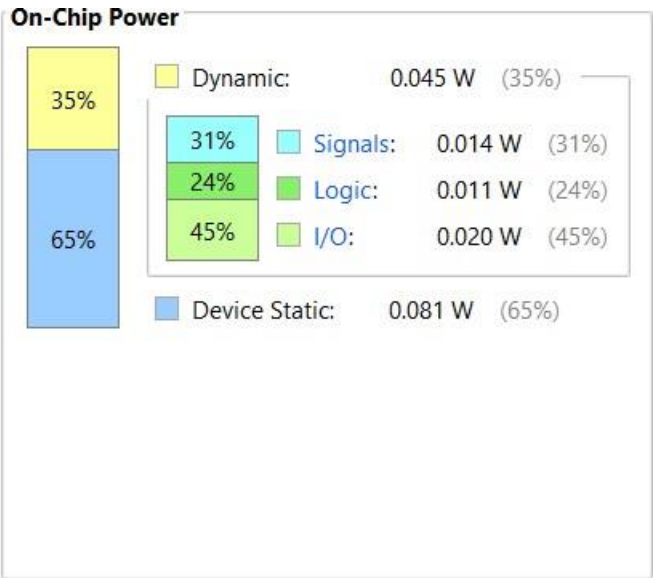[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



25.N:1 MUX







Verilog code:

```
module mux_4_1(  
    input [1:0] sel,  
    input i0,i1,i2,i3,  
    output reg y);  
  
    always @(*) begin  
        case(sel)  
            2'h0: y = i0;  
            2'h1: y = i1;  
            2'h2: y = i2;  
            2'h3: y = i3;  
            default: $display("Invalid sel input");  
        endcase  
    end  
endmodule
```


Testbench:

```
module tb;  
    reg [1:0] sel;  
    reg i0,i1,i2,i3;  
    wire y;  
  
    mux_4_1 mux(sel, i0, i1, i2, i3, y);  
  
    initial begin  
        $monitor("sel = %b -> i3 = %0b, i2 = %0b ,i1 = %0b, i0 = %0b -> y = %0b", sel,i3,i2,i1,i0, y);  
        {i3,i2,i1,i0} = 4'h5;  
        repeat(6) begin  
            sel = $random;  
            #5;  
        end  
    end  
endmodule
```

Simulation:

  Name	Value	0.000 ns	20.000 ns	40.000 ns	60.000 ns	80.000 ns	100.000 ns	120.000 ns	140.000 ns
 sel[1:0]	1	0	1	3					1
 i0	1								
 i1	0								
 i2	1								
 i3	0								
 y	0								

Schematic:

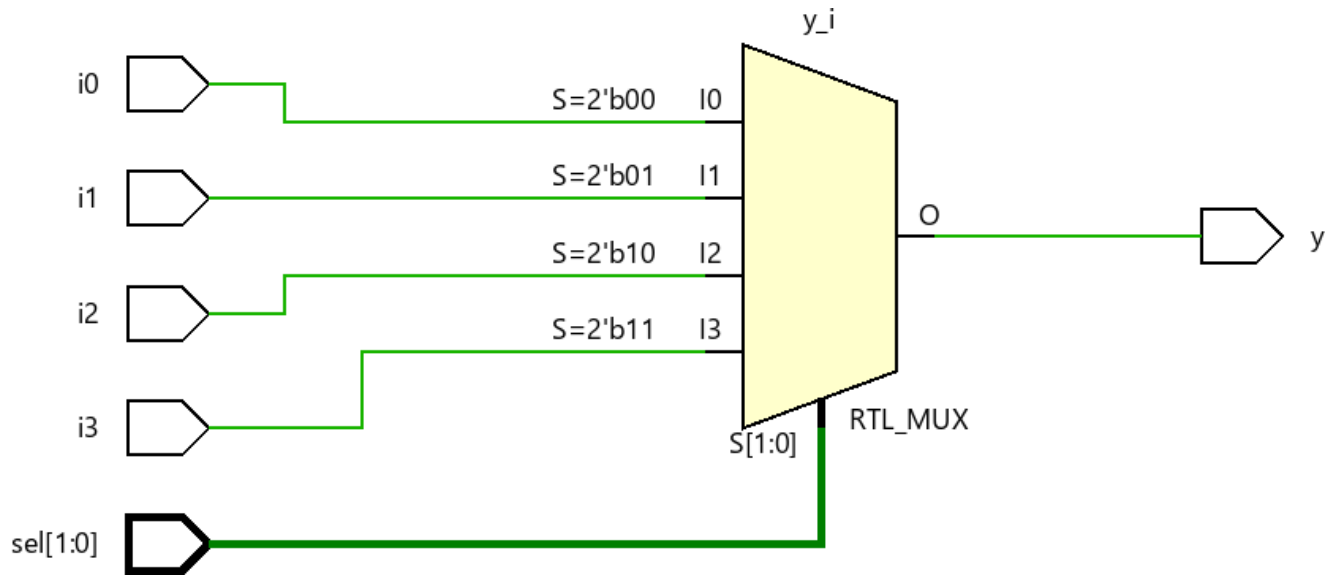

Synthesis report:

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| |BlackBox name |Instances |
+-----+
+-----+
```

Report Cell Usage:

```
+-----+-----+
|      |Cell |Count |
+-----+-----+
| 1     |LUT6 |    1|
| 2     |IBUF |    6|
| 3     |OBUF |    1|
+-----+-----+
```

Report Instance Areas:

```
+-----+-----+-----+
|      |Instance |Module |Cells |
+-----+-----+-----+
| 1     |top      |      |    8|
+-----+-----+-----+
```

Finished Writing Synthesis Report

Power report:

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.535 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	26.0°C
Thermal Margin:	59.0°C (31.1 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

